



Physics 2: Electricity , Optics and Quanta

Week 4 - Capacitor

2023.9

QQ group: 776916994

cyjing@swjtu.edu.cn


Outline

Basic properties of capacitor

- Connection in circuit

Charging or discharging a capacitor

Capacitors

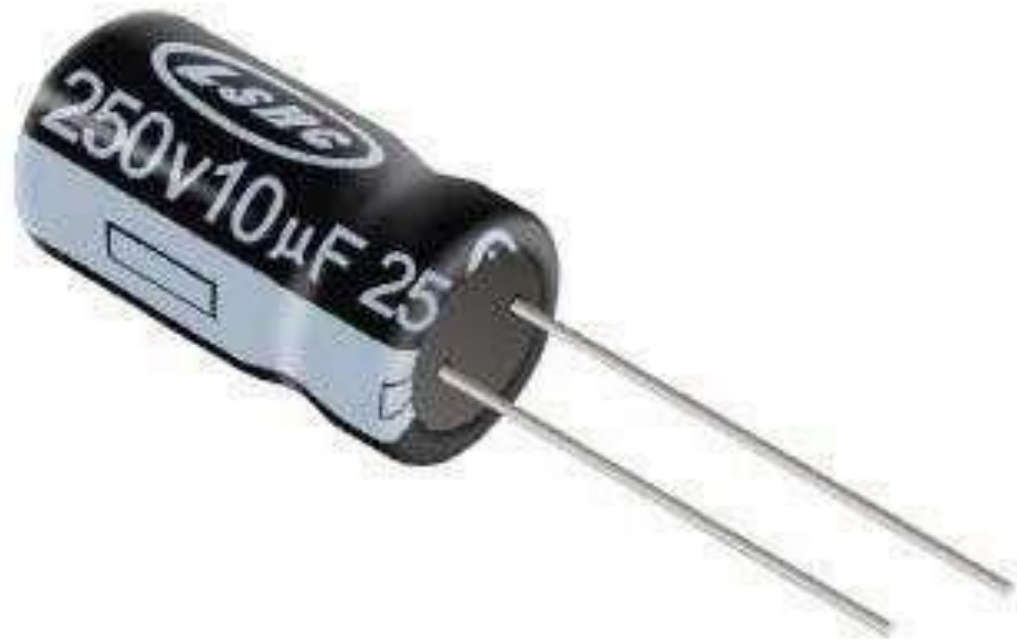

$$Q = CV$$

$$Q = \frac{A\epsilon_0}{D} \Delta V$$

capacitance

$$E \rightarrow \sigma \rightarrow Q \rightarrow V \Rightarrow C - \epsilon_r$$

Capacitors


$$Q = \frac{A\epsilon_0}{D} \Delta V$$

the charge on the plate(s) is **proportional** to the voltage



The coefficient is called the “**capacitance**”

$$C = \frac{Q}{\Delta V}$$

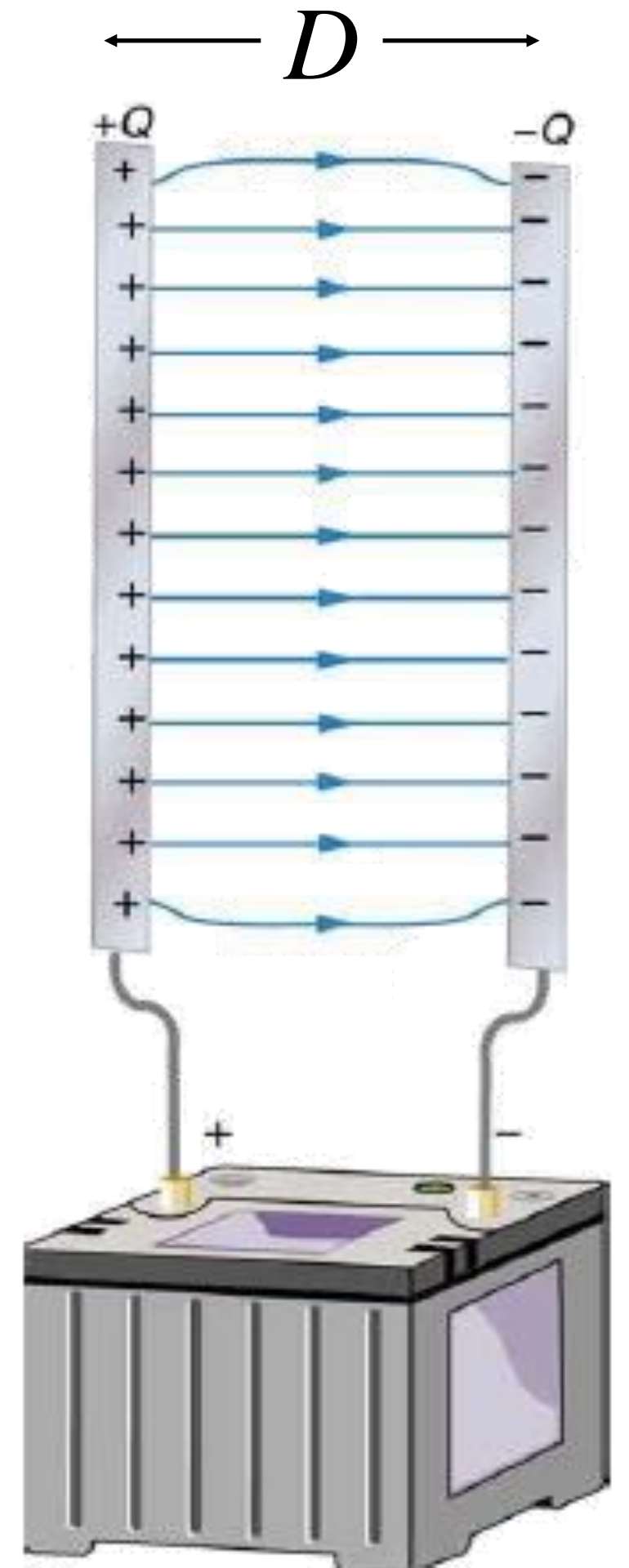For parallel-plates $C = \frac{A\epsilon_0}{D}$



Different shapes of capacitors

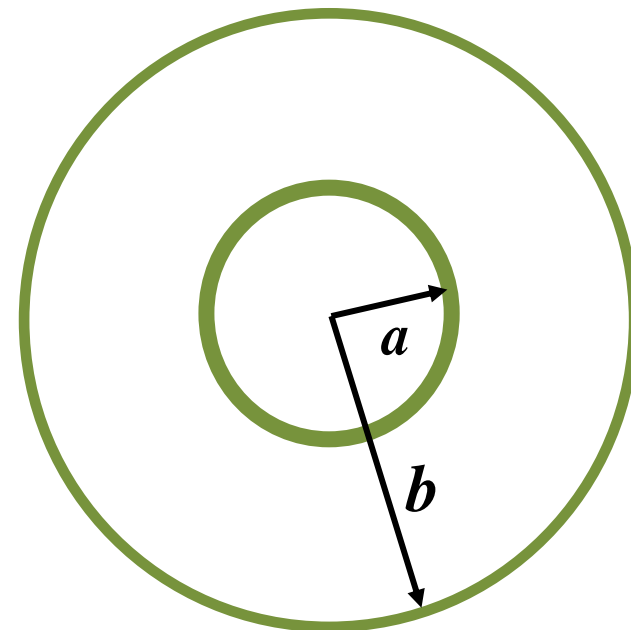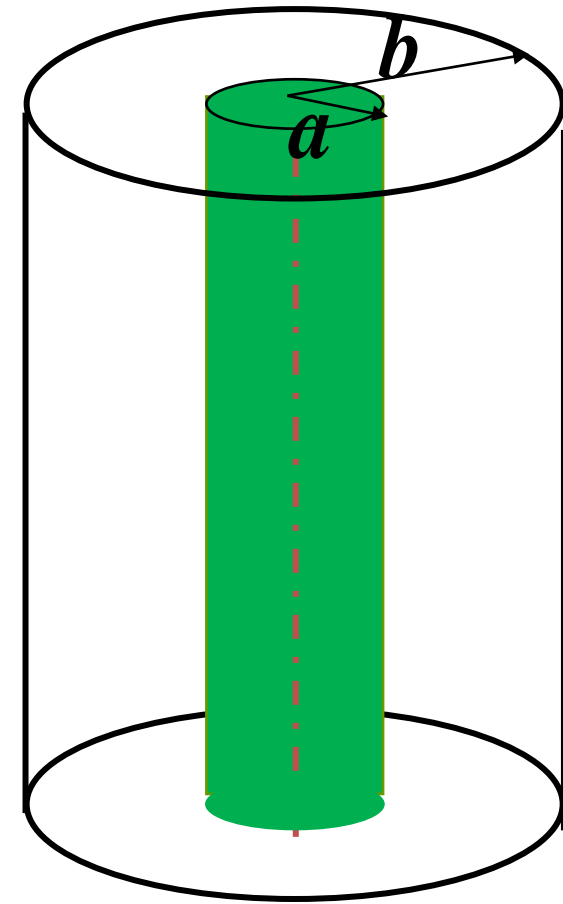

C depends on?

$$C = \frac{Q}{V}$$

Units – farad (F)

$$1\text{ F} = \frac{1\text{ Coulomb}}{1\text{ Volt}}$$

Different shapes of capacitors

$$C = \frac{Q}{V}$$

$$C = \frac{A\epsilon_0}{D}$$

C depends on


charge

voltage

geometry of plates

relative position

dielectric

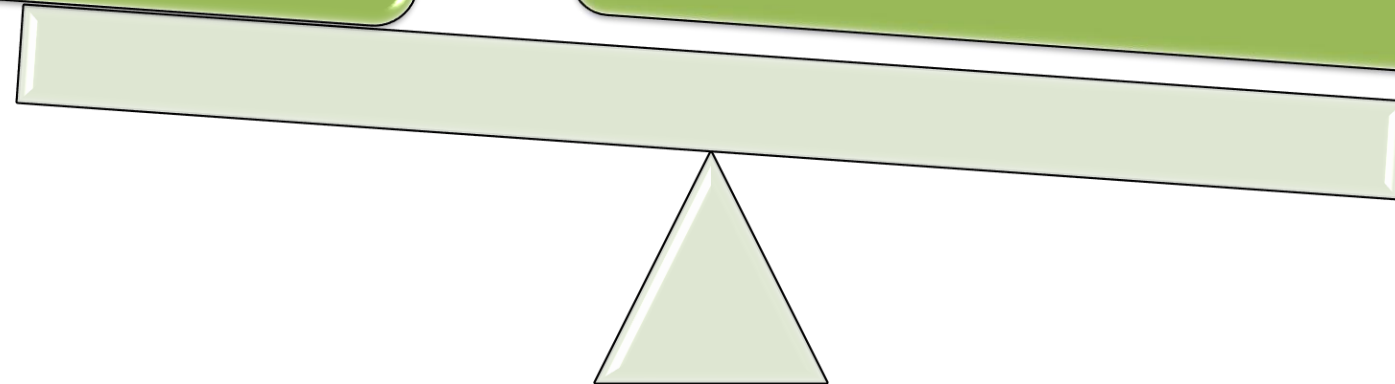



Capacitors

Electrolytic capacitors

non-solid (wet)




Ceramic capacitors

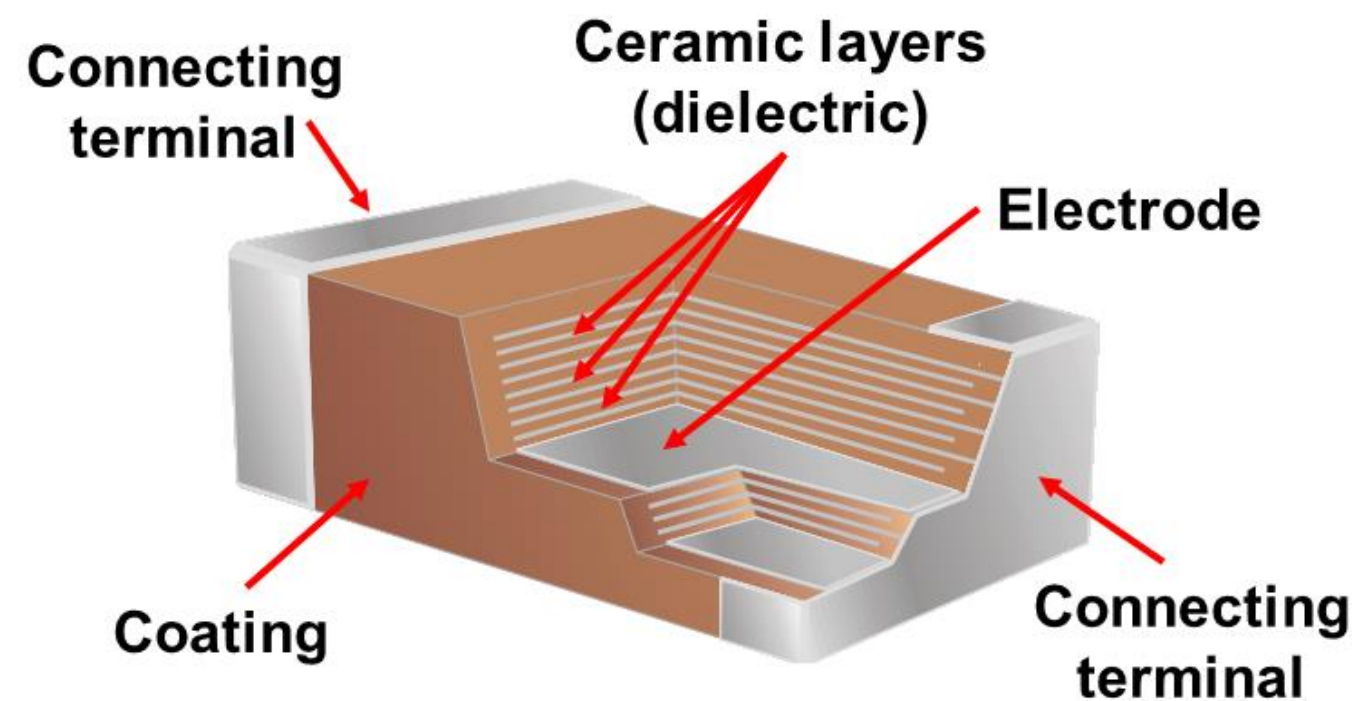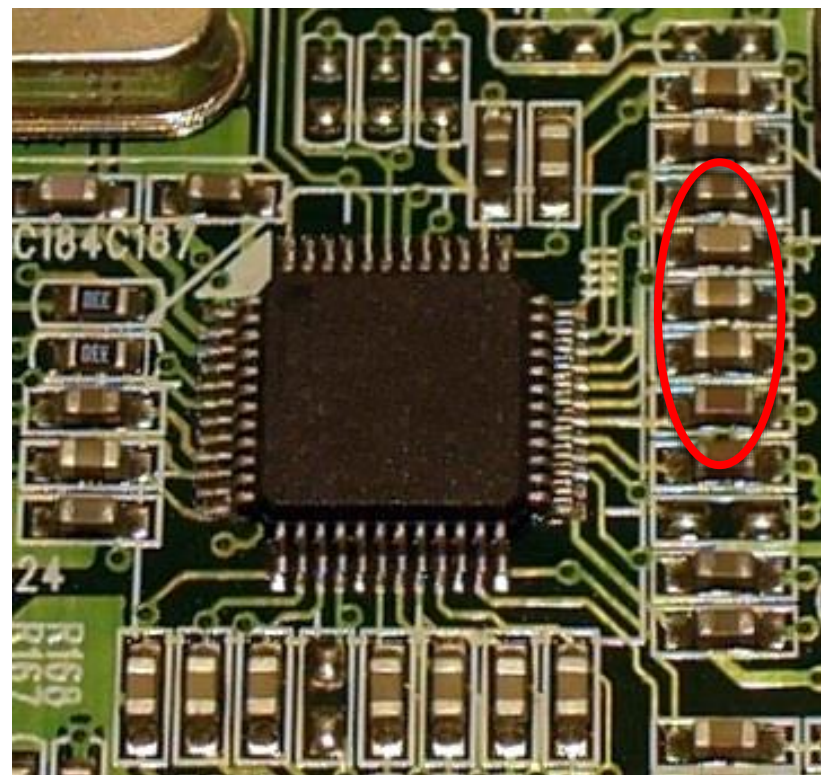


solid

Connecting capacitors “in series”

What is the
“equivalent” capacitance ?

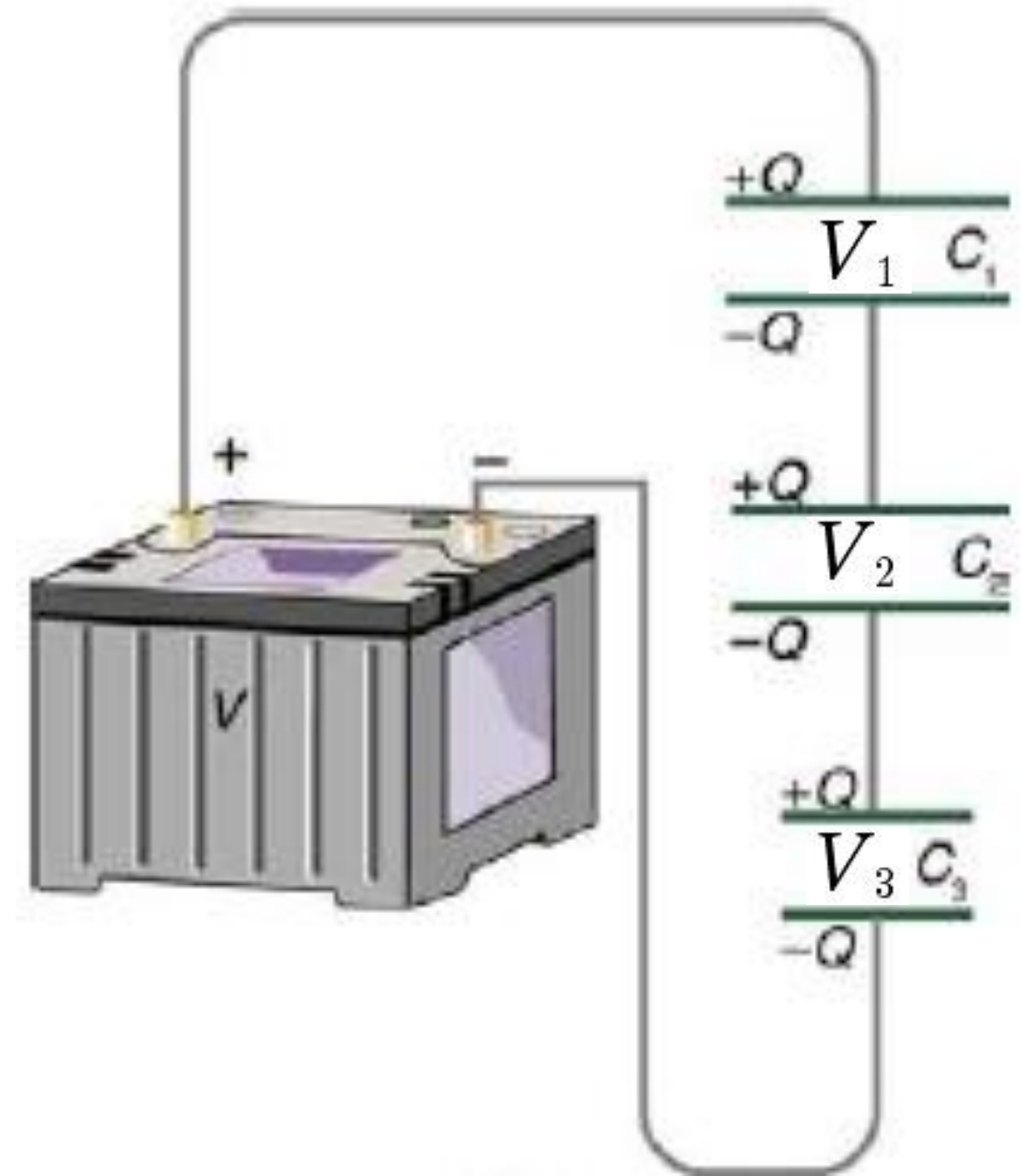

Connecting capacitors “in series”

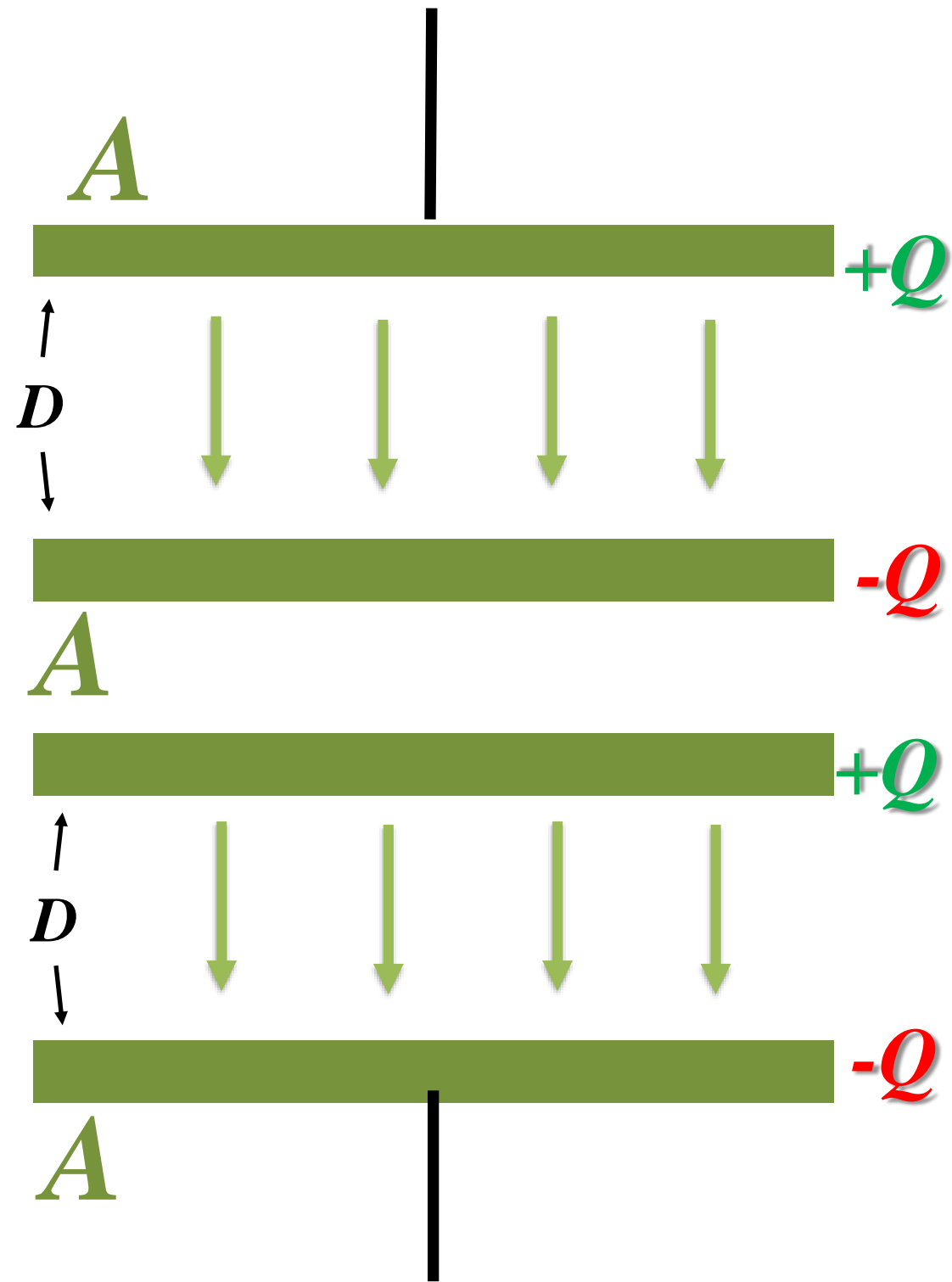


$$C = \frac{A\epsilon_0}{D}$$

$$D \rightarrow 2D$$

$$C \rightarrow C/2$$

$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C}$$

Capacitance change

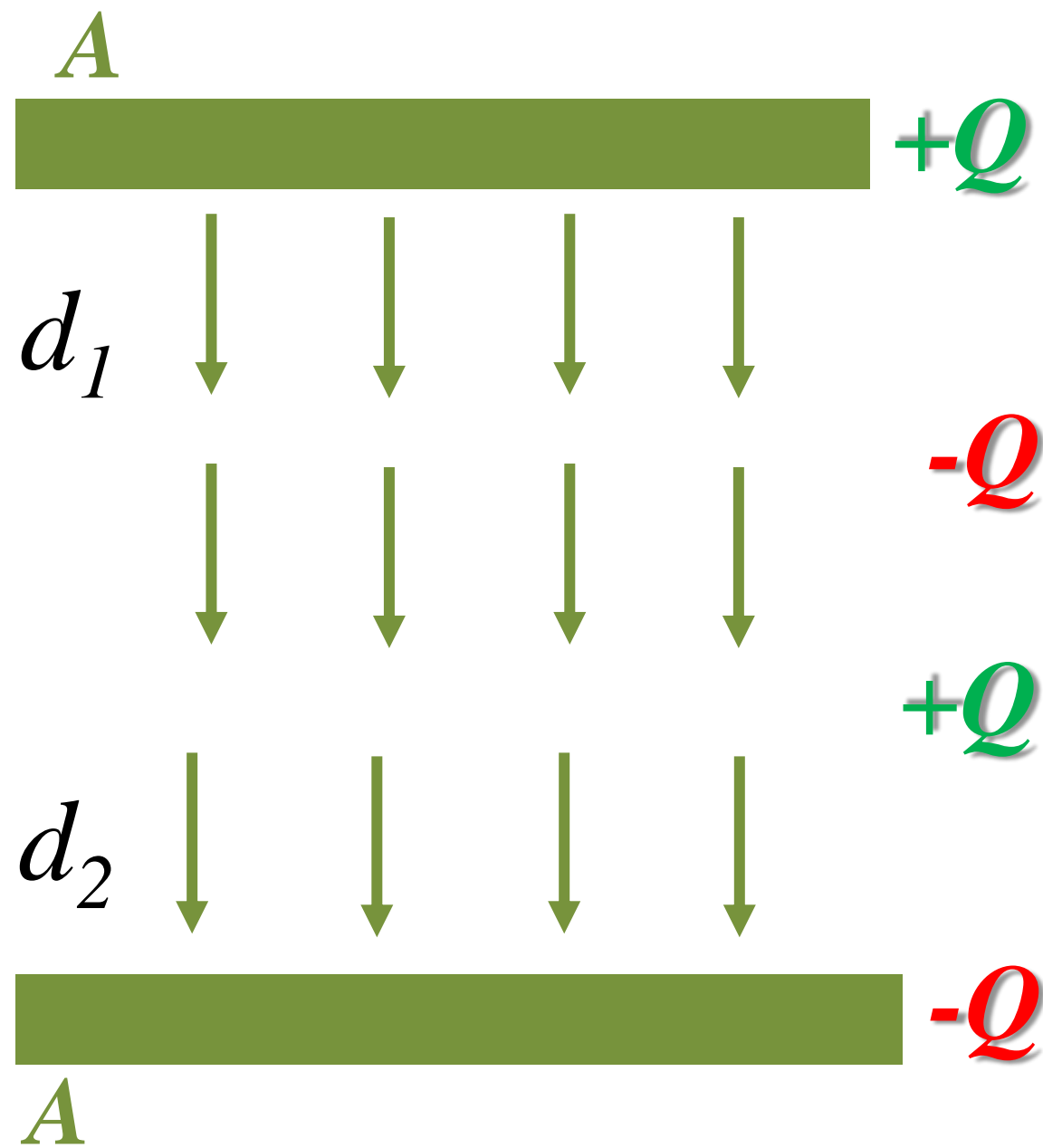

How will the capacitance change after the insertion of a piece of metal?




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{d_1 + d_2}{A\epsilon_0}$$


$$C_{eq} = \frac{A\epsilon_0}{d_1 + d_2} > C = \frac{A\epsilon_0}{D}$$

Connecting capacitors “in parallel”

What is the
“equivalent” capacitance ?

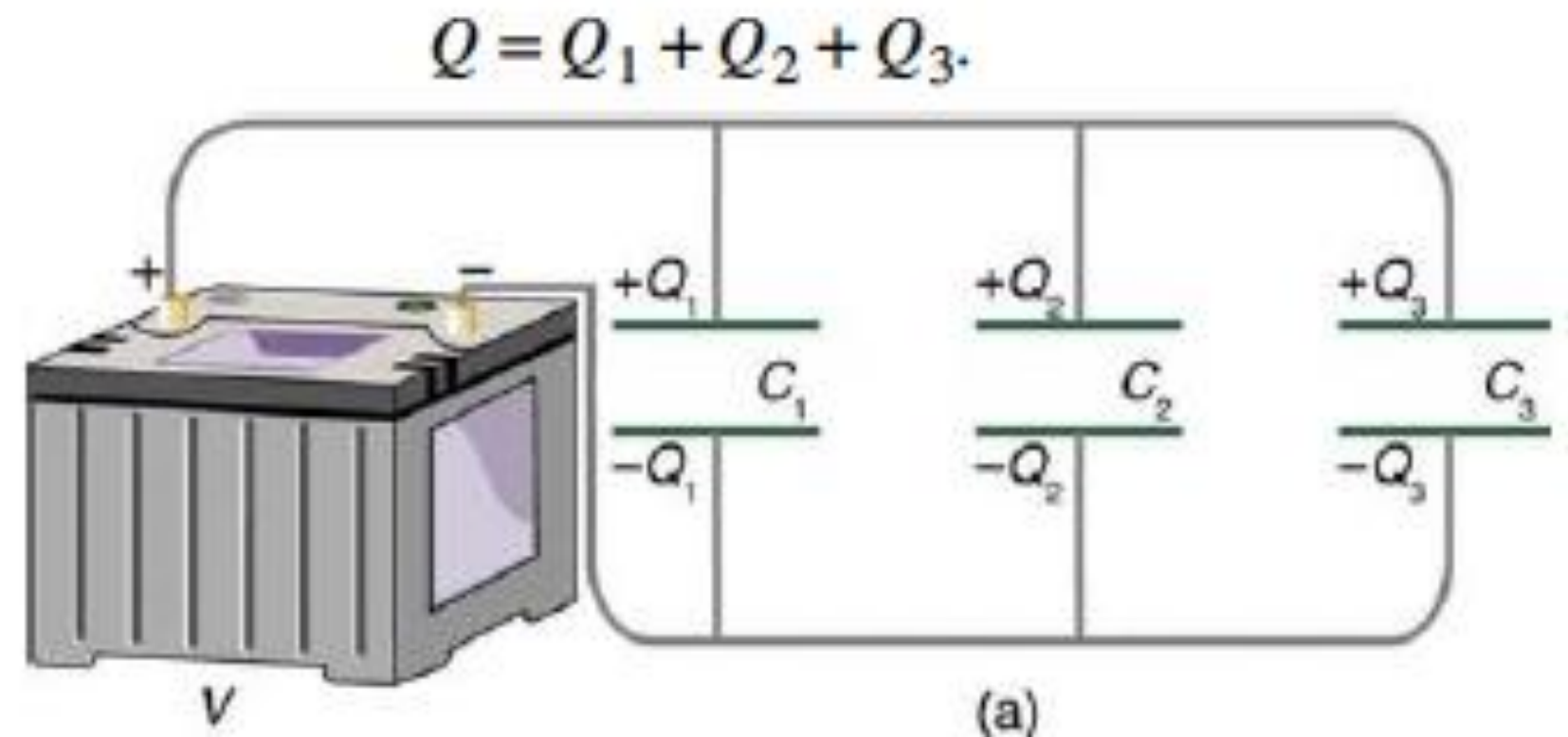


Connecting capacitors “in parallel”

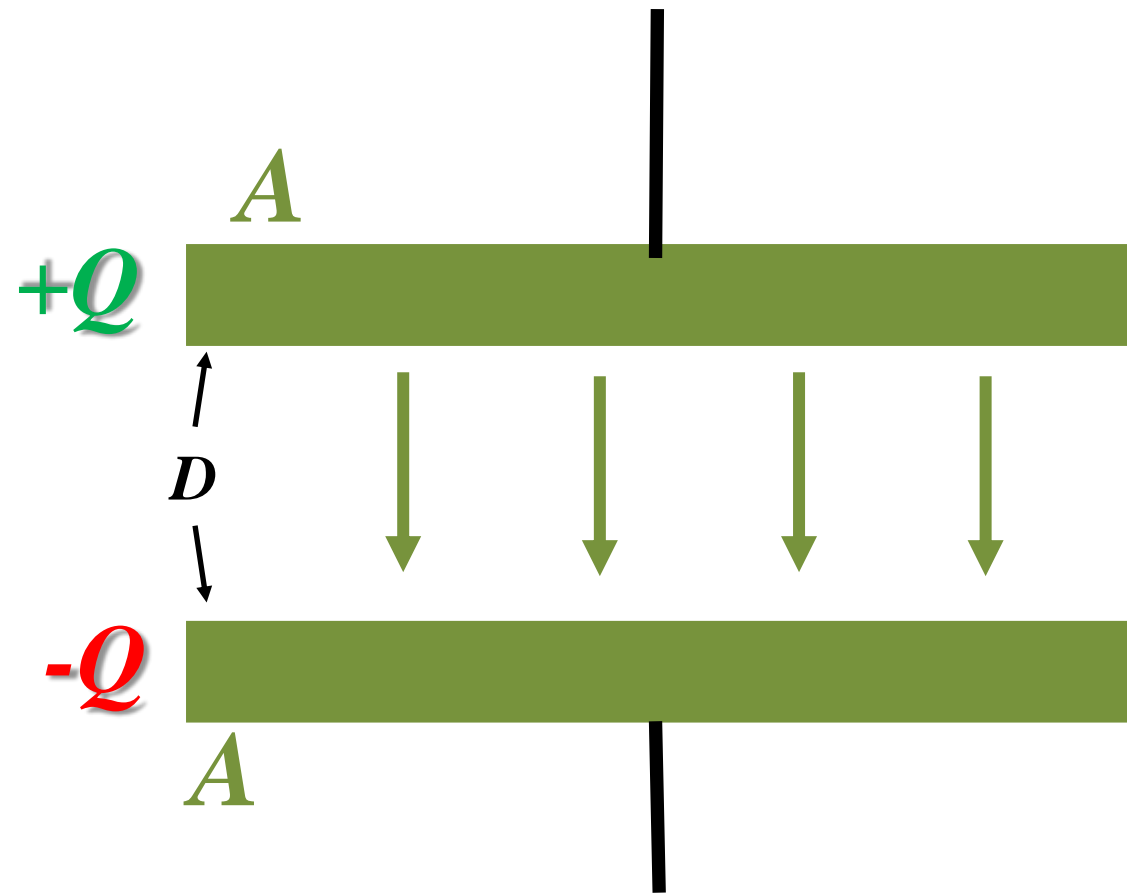

$$C = \frac{A\epsilon_0}{D}$$

$$A \rightarrow 2A$$


$$C_{eq} = C + C$$

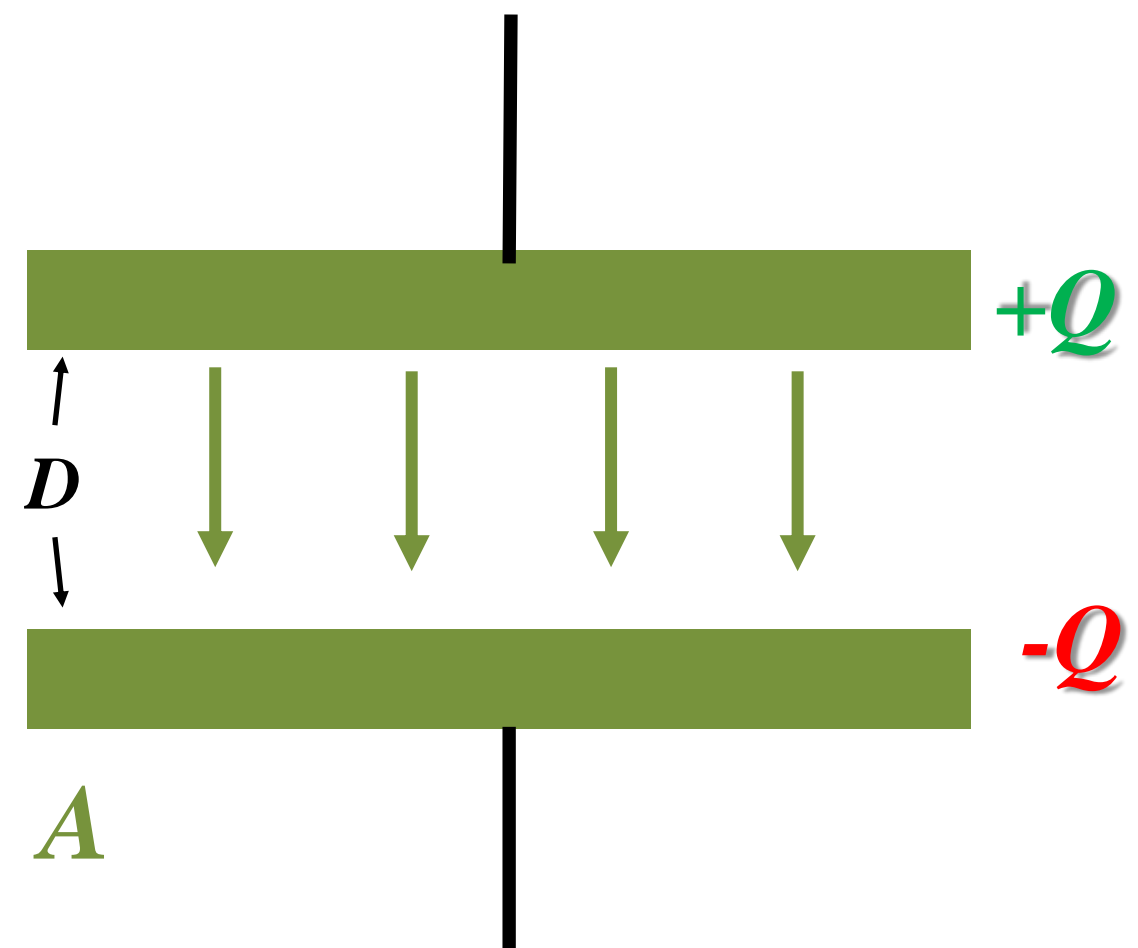

$$C \rightarrow 2C$$

Energy of the Capacitor

$$Q = ne \quad -Q = -ne$$

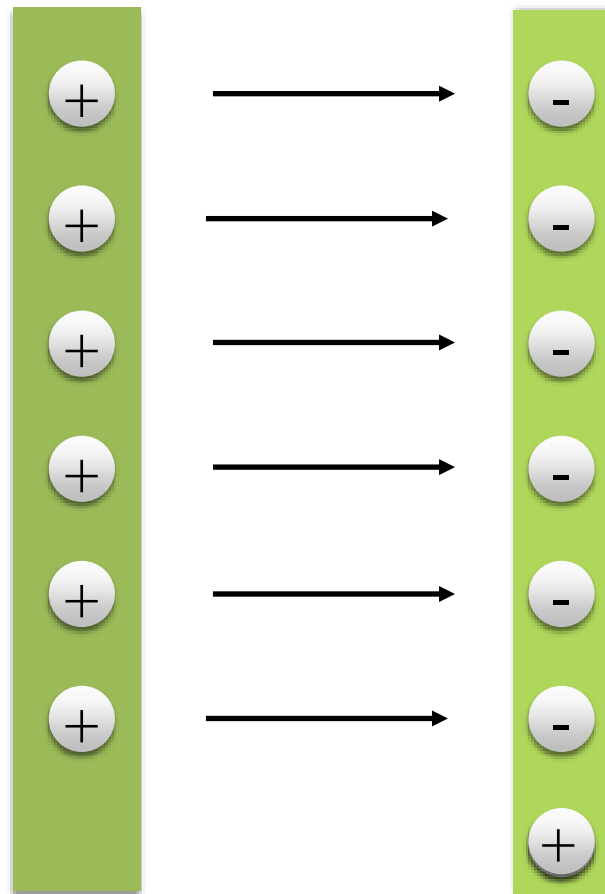


An energy is needed!

What is the energy stored in the Capacitor?

- Energy is required to bring a charge from one plate to the other, due to the electric force doing (negative) work
- The energy stored is the sum of the energy required to move all of the charges.

Energy of the Capacitor

$$Q = ne \quad -Q = -ne$$

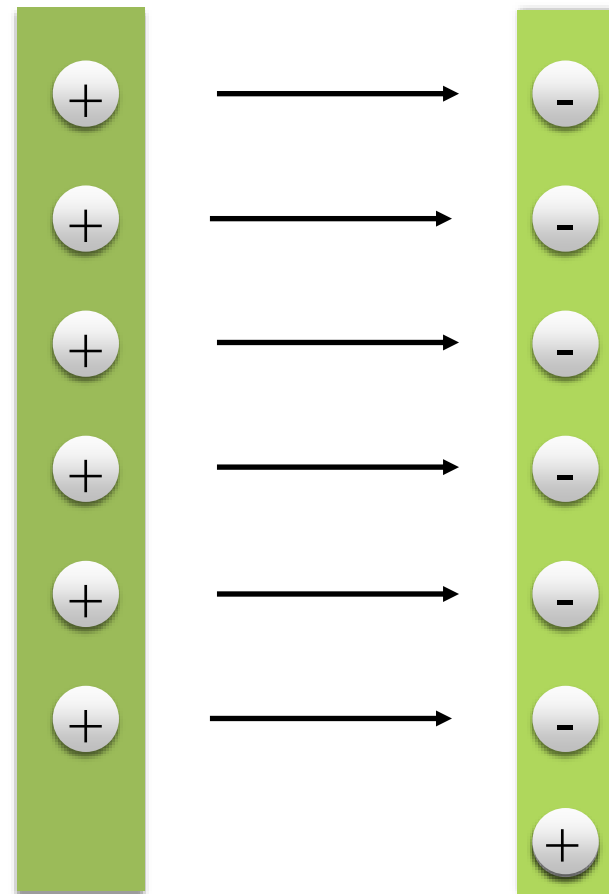

An energy of eV_{tot} is needed!


Capacitor with charge $Q = ne$

e = elementary charge

$$V_{tot} = \frac{Q}{C} = \frac{ne}{C}$$

- More energy is required when voltage is higher
- As you add charges, you need more and more energy to move a charge

Energy of the Capacitor

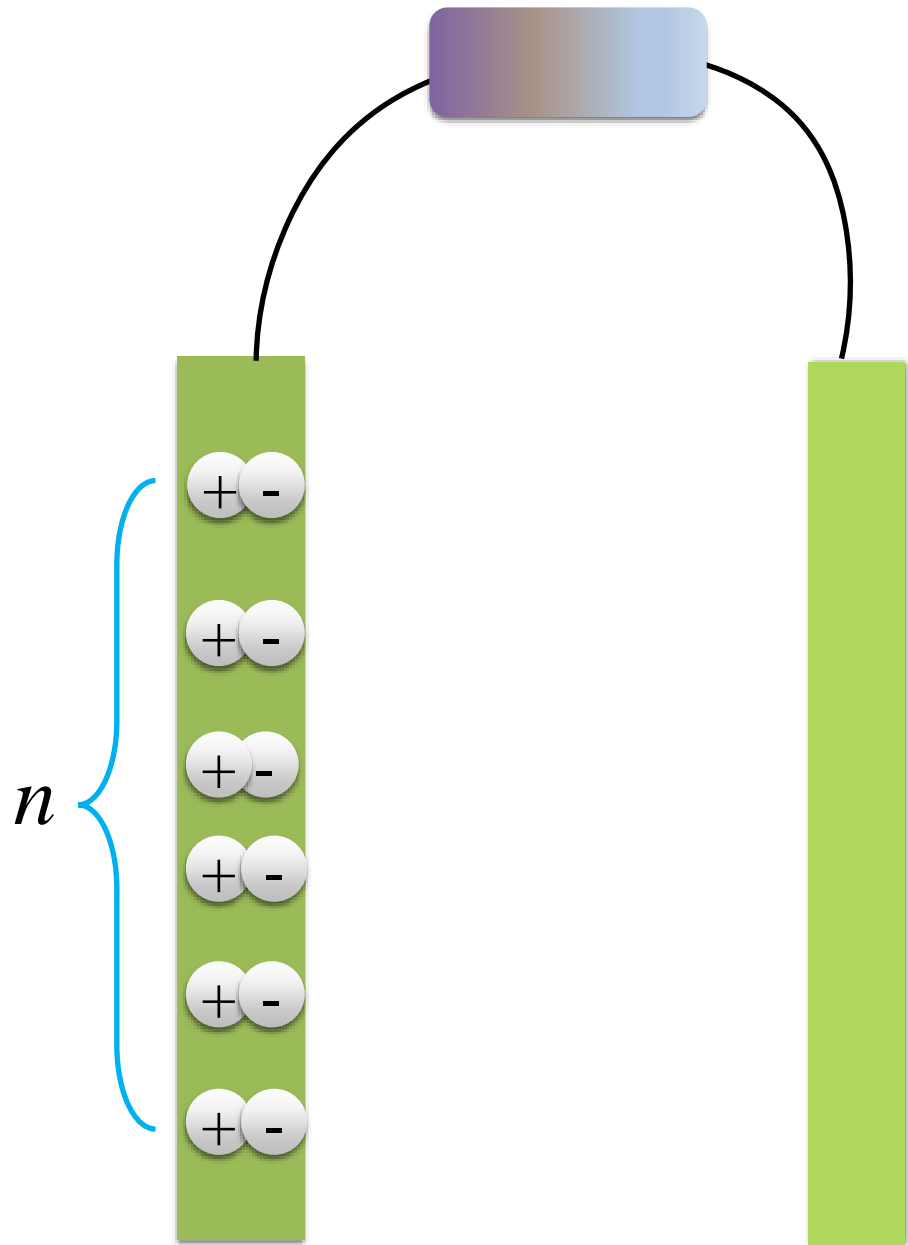


charge number	voltage across plates	energy required
1	$V = 0$	$eV = 0$
2	$V_1 = \frac{e}{C} = \frac{Q}{nC} = \frac{V_{tot}}{n}$	$eV_1 = \frac{eV_{tot}}{n}$
3	$V_2 = \frac{2V_{tot}}{n}$	$eV_2 = \frac{2eV_{tot}}{n}$
	\vdots	\vdots
n	$V_n = \frac{(n-1)V_{tot}}{n} \approx V_{tot}$	$eV_n = \frac{(n-1)eV_{tot}}{n}$ $\approx eV_{tot}$

Energy of the Capacitor

charge number	voltage across plates	energy required
1	$V = 0$	$eV = 0$
2	$V_1 = \frac{e}{C} = \frac{Q}{nC} = \frac{V_{tot}}{n}$	$eV_1 = \frac{eV_{tot}}{n}$
3	$V_2 = \frac{2V_{tot}}{n}$	$eV_2 = \frac{2eV_{tot}}{n}$
	\vdots	\vdots
	$V_n = \frac{(n-1)V_{tot}}{n} \approx V_{tot}$	$eV_n = \frac{(n-1)eV_{tot}}{n} \approx eV_{tot}$

Energy added

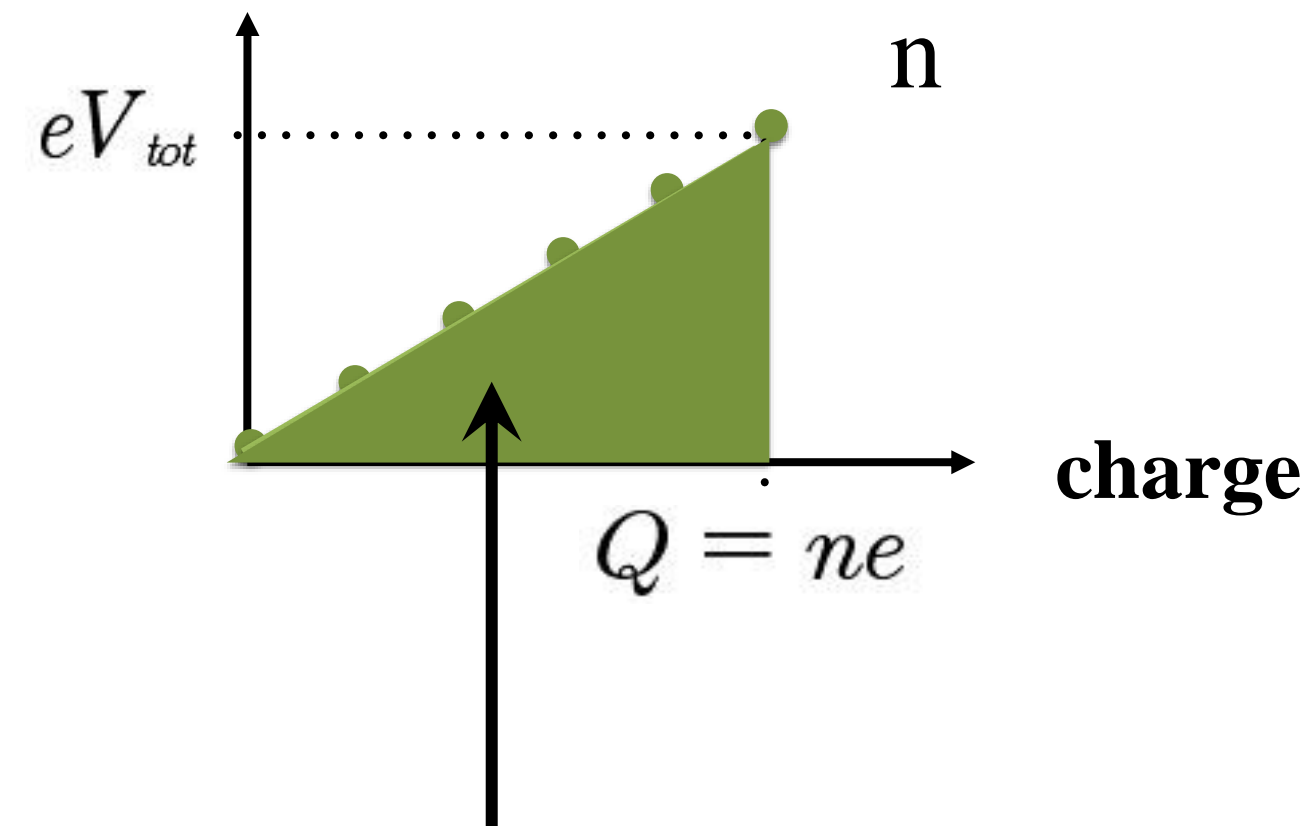

Total energy added

Energy of the Capacitor

The energy needed to add a charge dq is:

$$dW = V dq = \frac{q}{C} dq$$

The total energy added is:

$$\int dW = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$

Total energy stored in a capacitor:

$$E_{cap} = \frac{QV}{2} = \frac{CV^2}{2} = \frac{Q^2}{2C}$$

It is also the electric energy of a capacitor

Energy with dielectric


How will the energy stored in the capacitor change after the **dielectric** being **removed**?

$$E = \frac{1}{2} CV^2$$

$$C = \frac{A\epsilon}{D}$$

$$E = \frac{A\epsilon}{2D} V^2$$
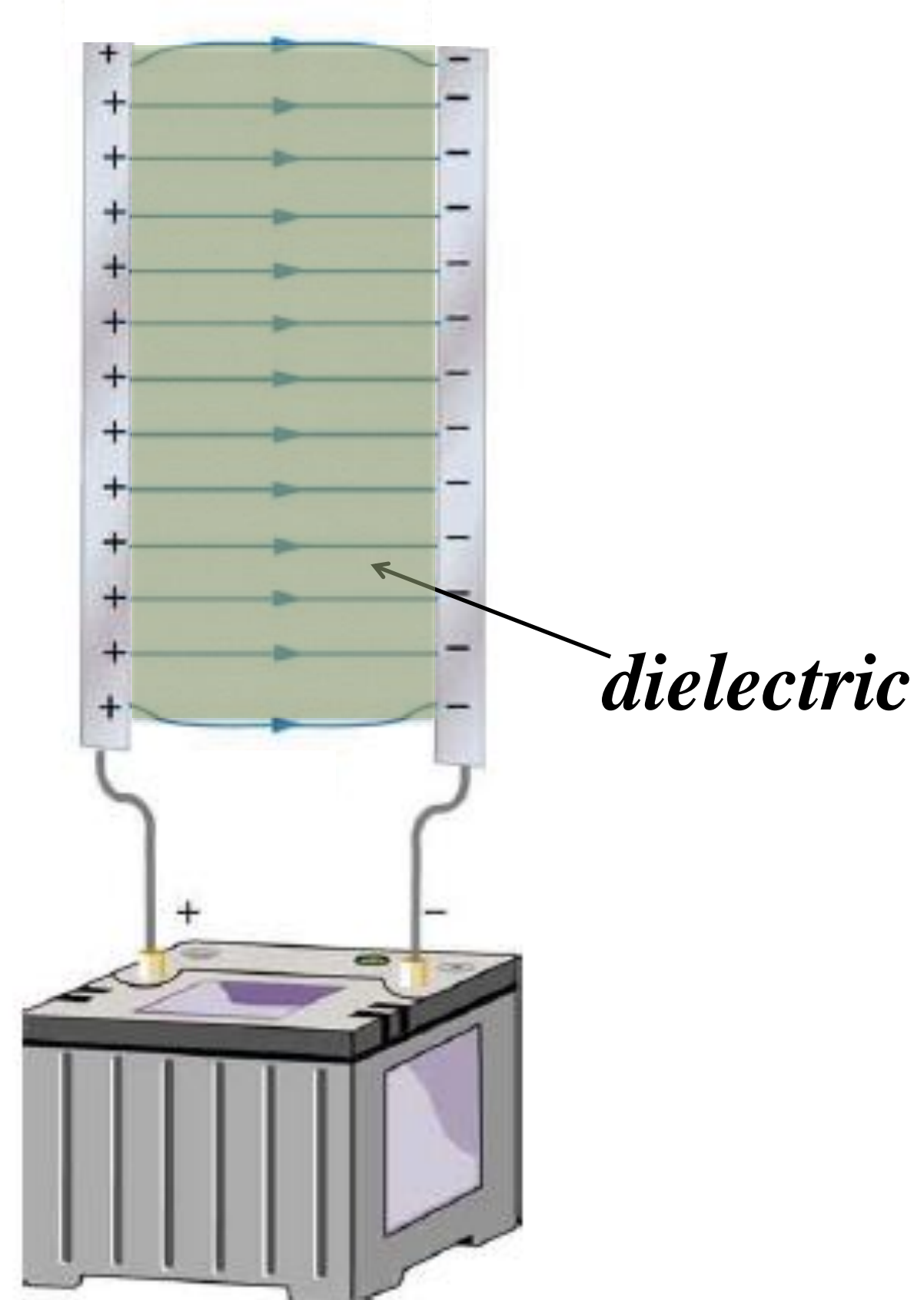
$$\epsilon \downarrow \Rightarrow E \downarrow$$



Energy with dielectric


How will the energy stored in the capacitor change after the **dielectric** being **removed**?

$$E = \frac{Q^2}{2C}$$



$$C = \frac{A\epsilon}{D}$$

$$E = \frac{DQ^2}{2A\epsilon}$$

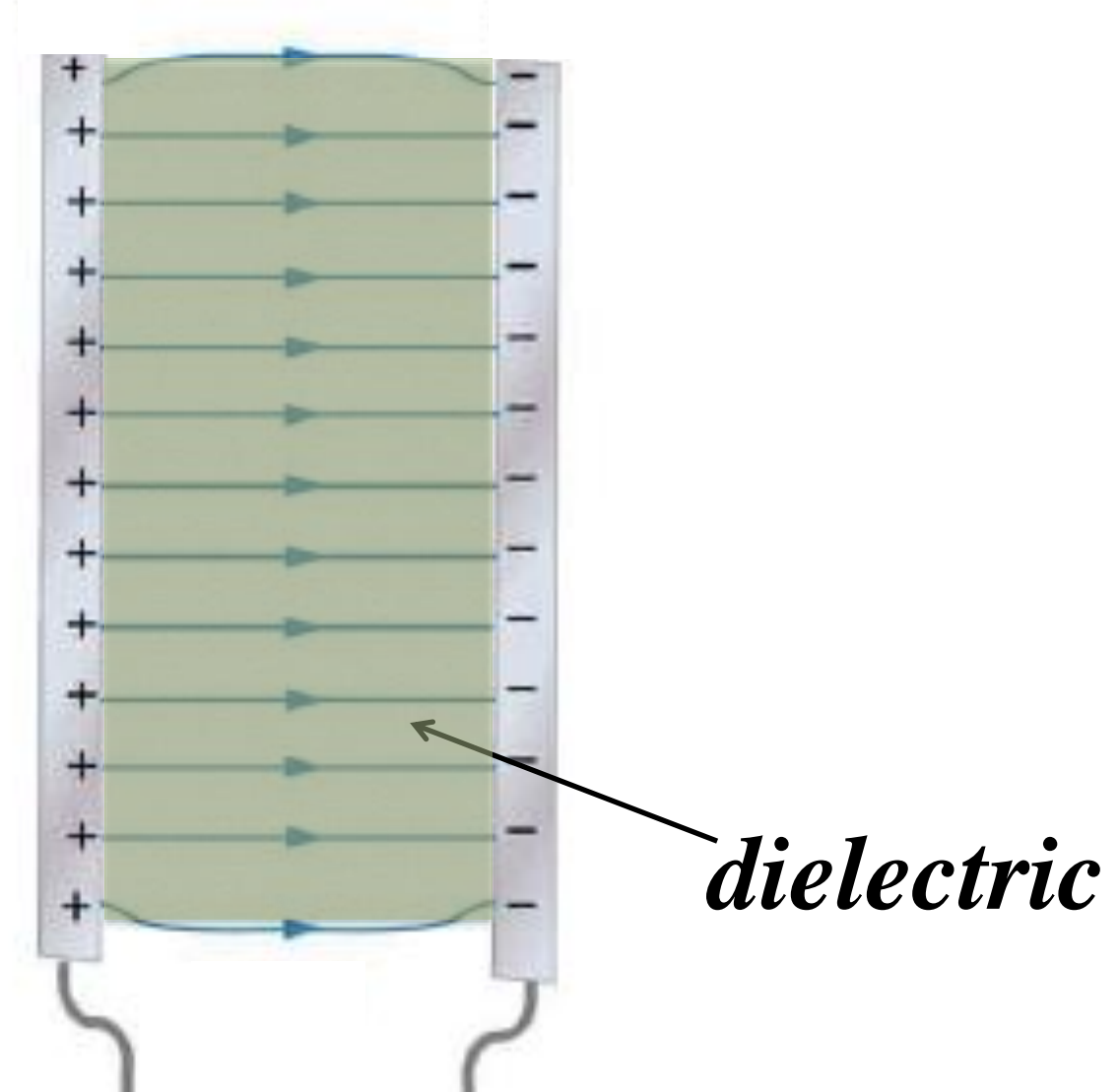
$$\epsilon \downarrow \Rightarrow E \uparrow$$




Energy with dielectric

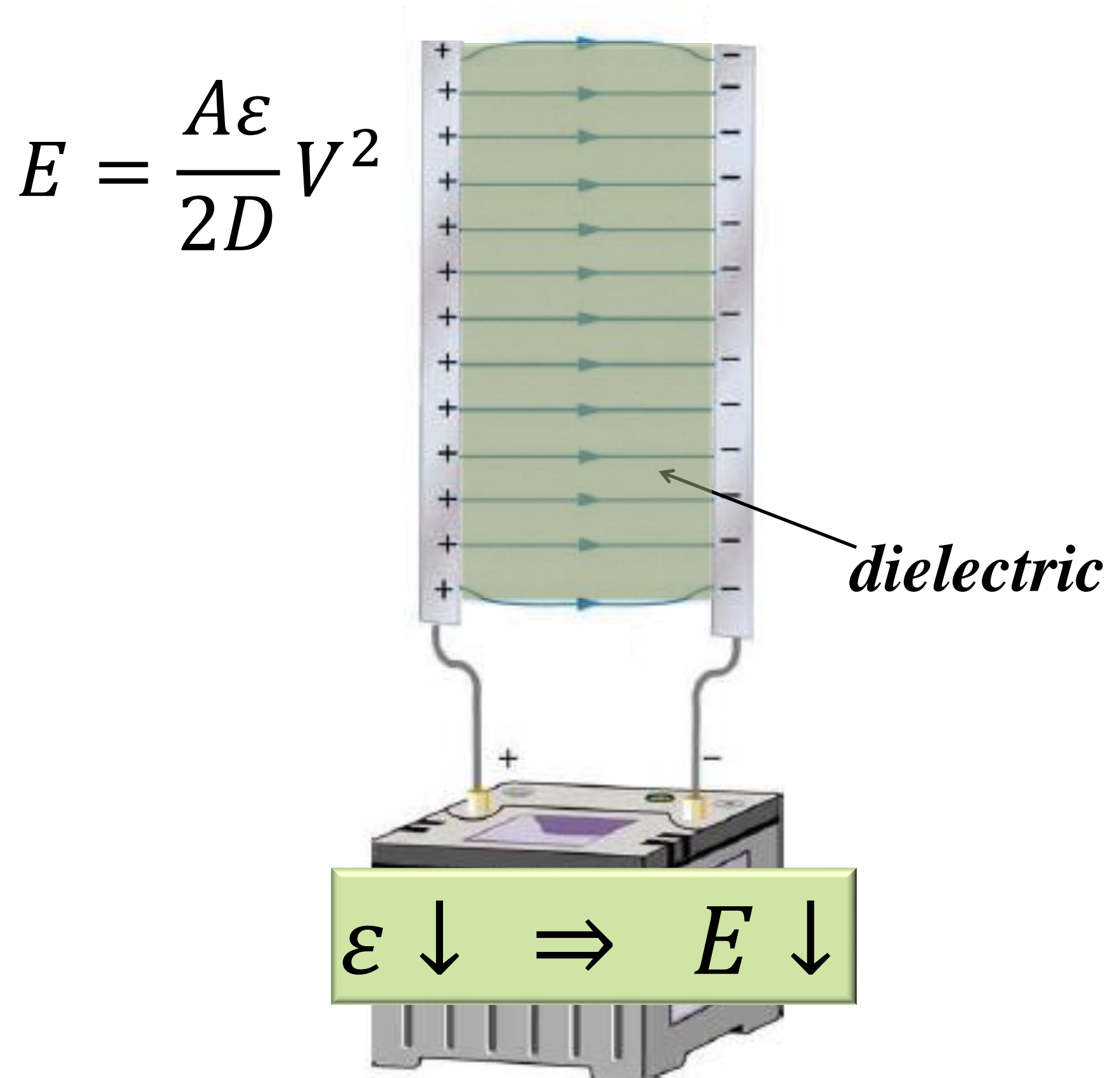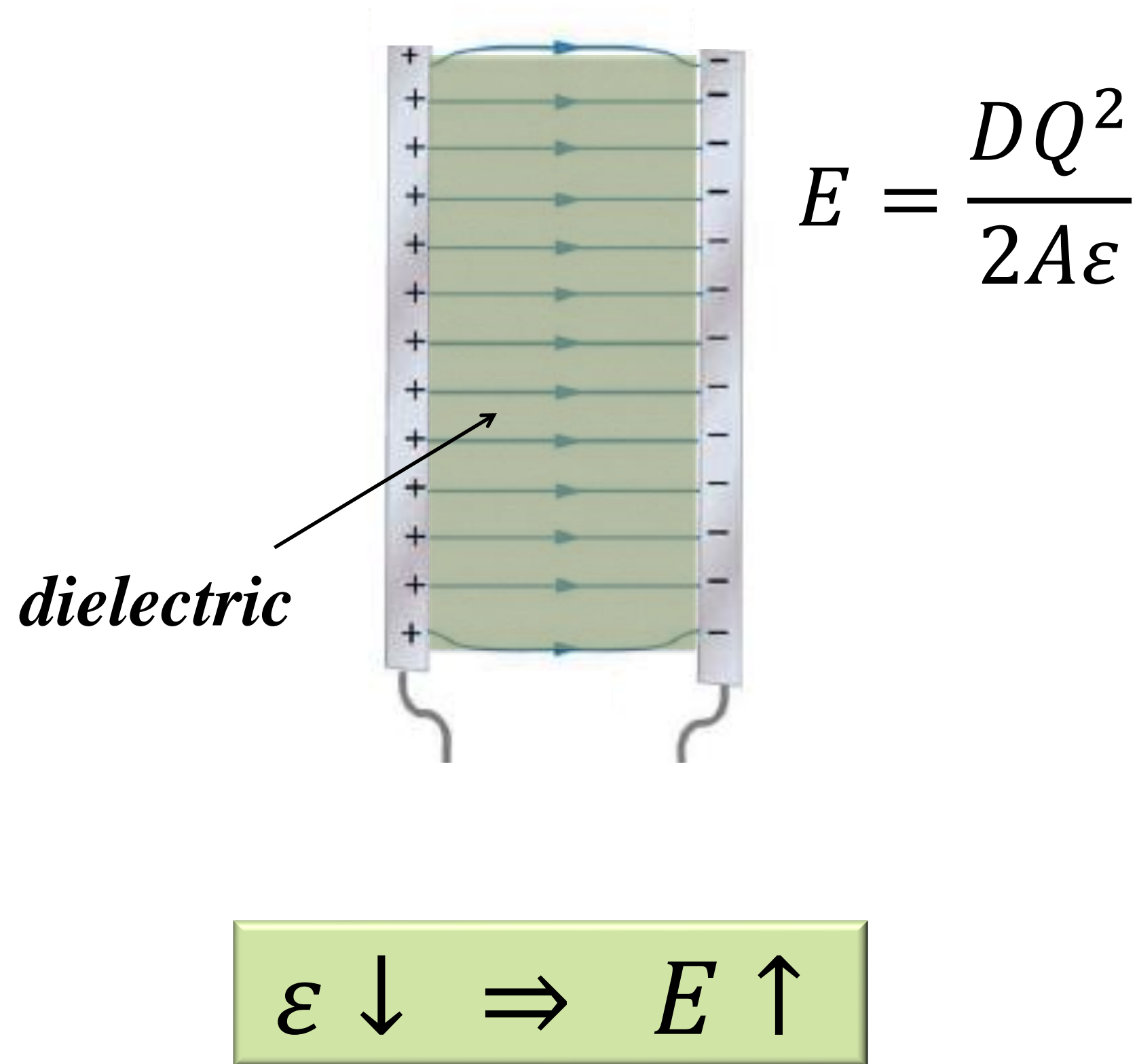

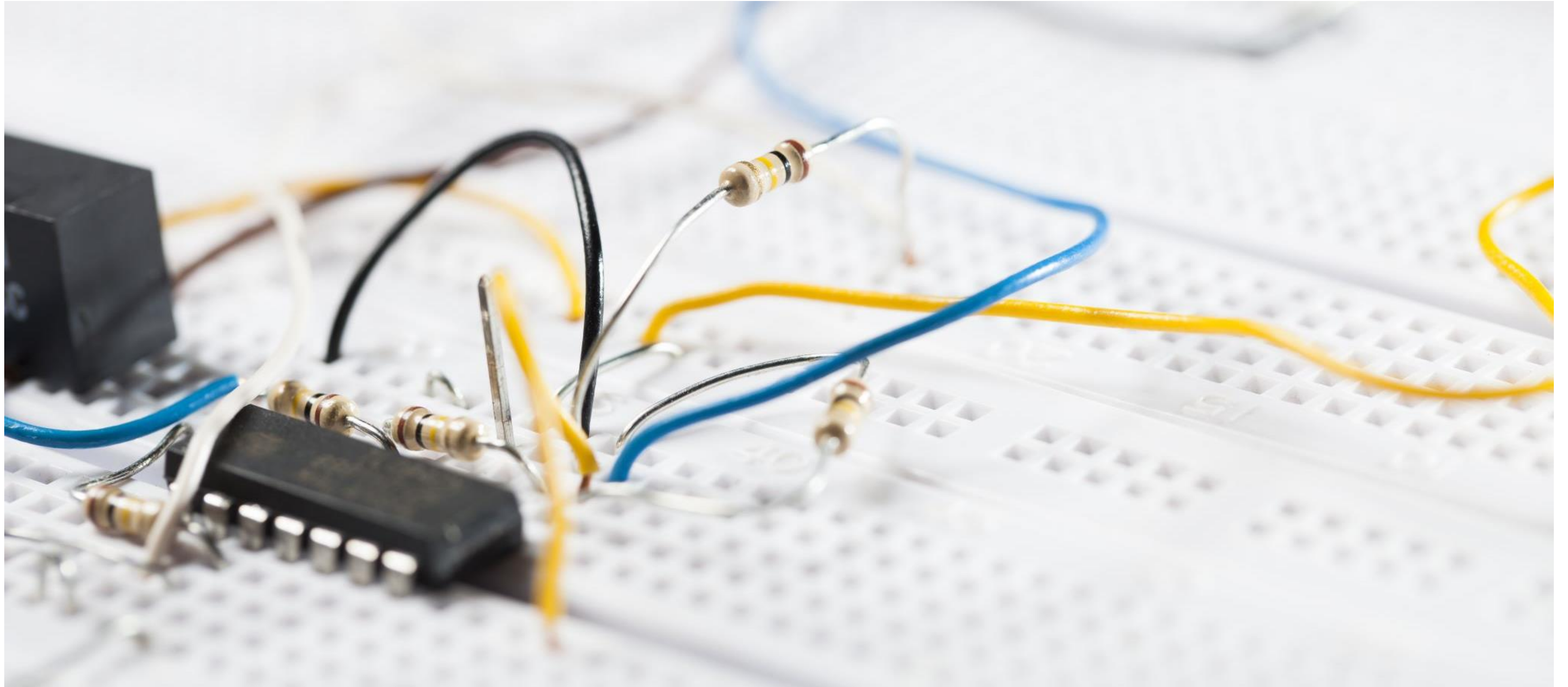The RC circuit & charging/discharging a capacitor




The RC circuit

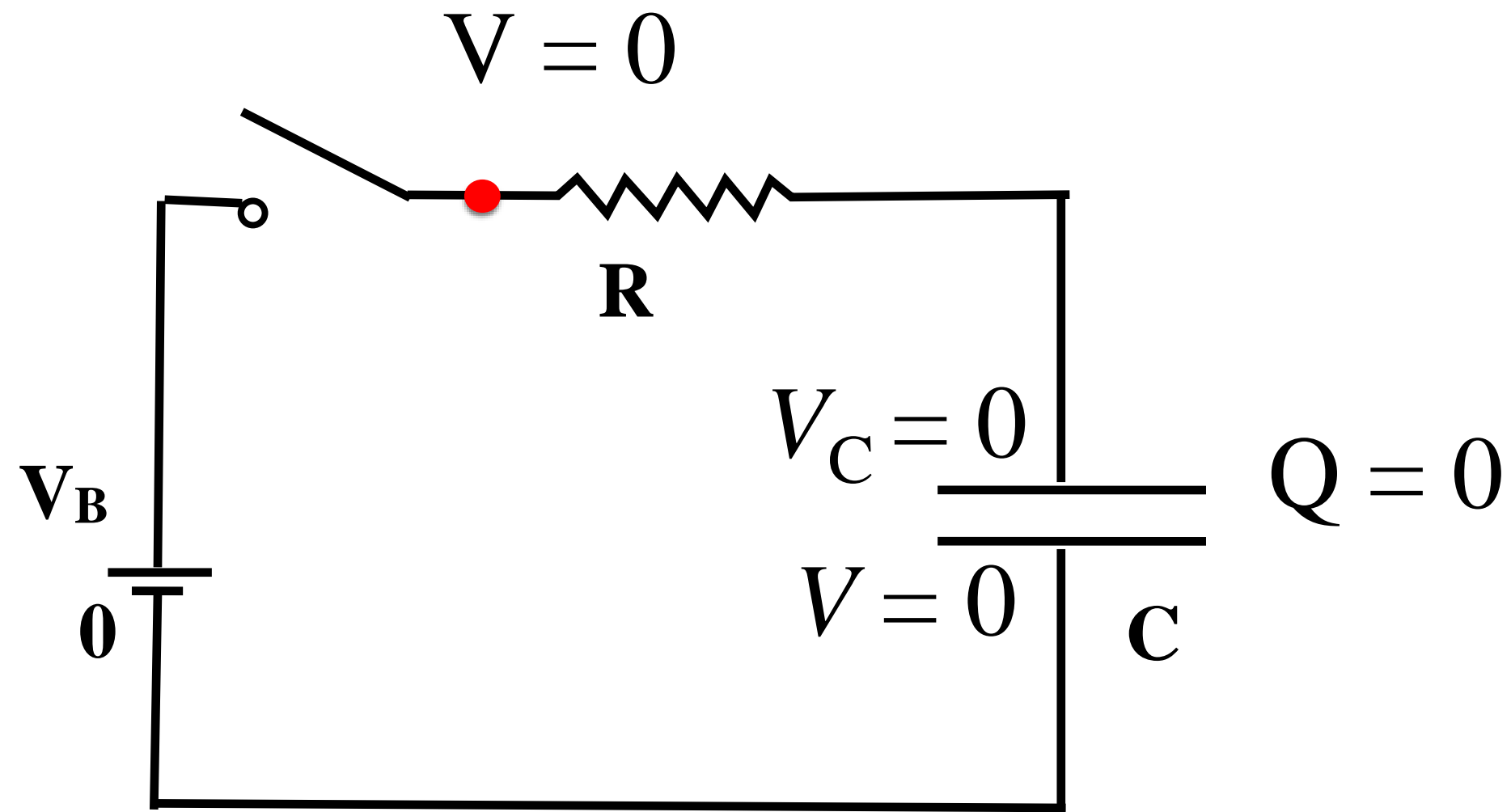


What happens when we close the switch?

The RC circuit

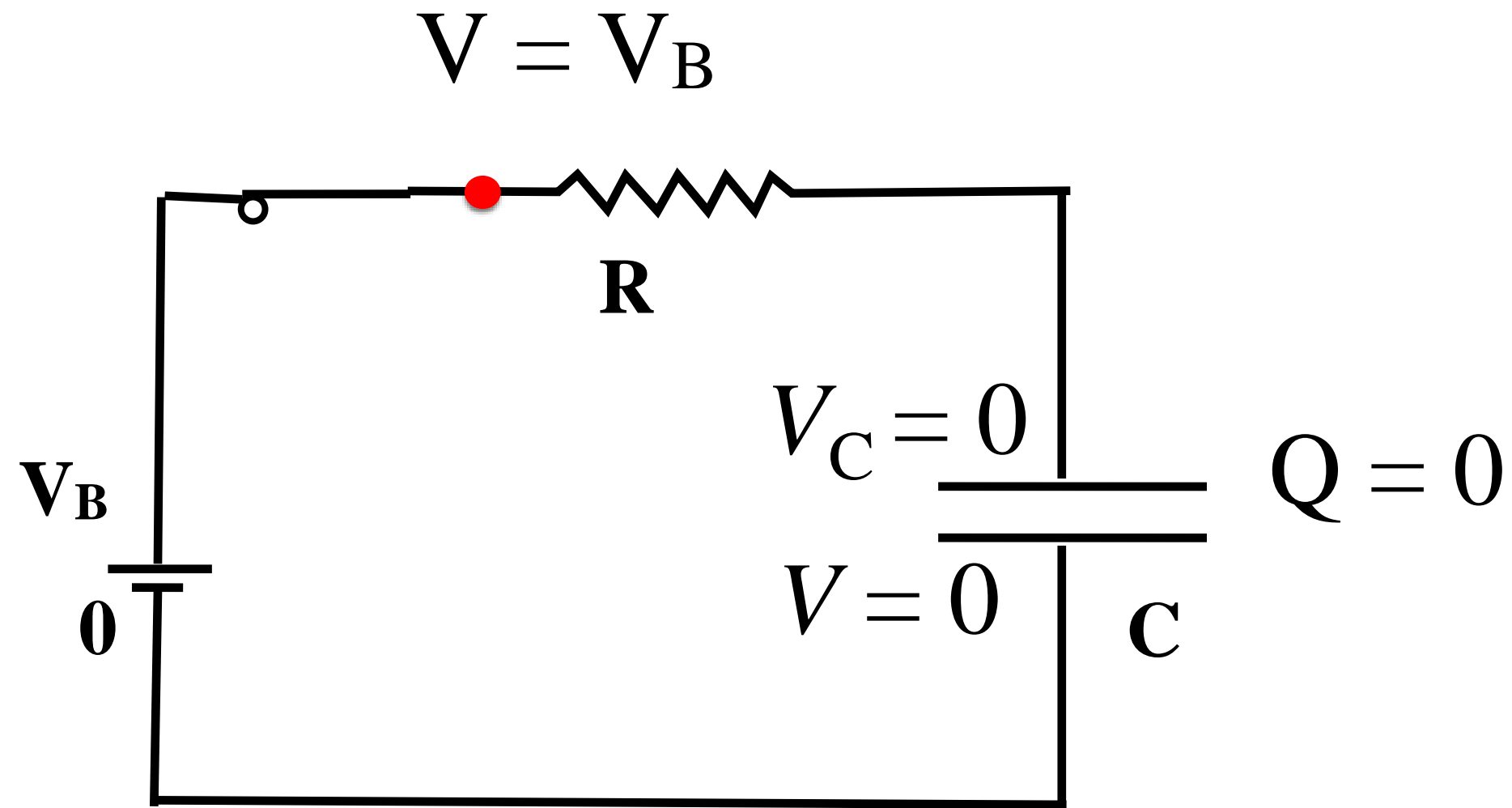

What happens when we close the switch?


The RC circuit

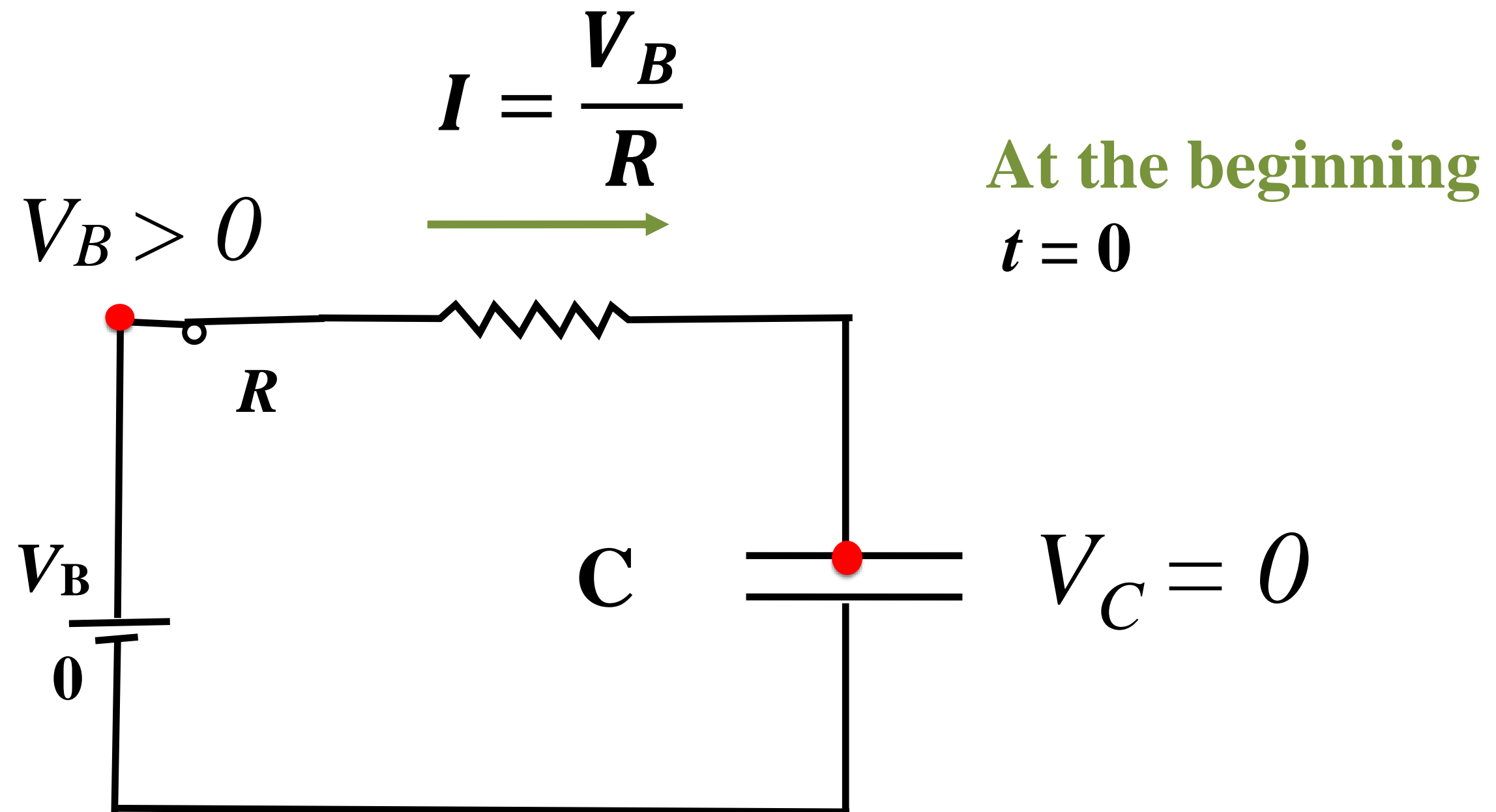

The RC circuit

$$I = \frac{V_B - V_C}{R} < \frac{V_B}{R}$$

later
 $t > 0$

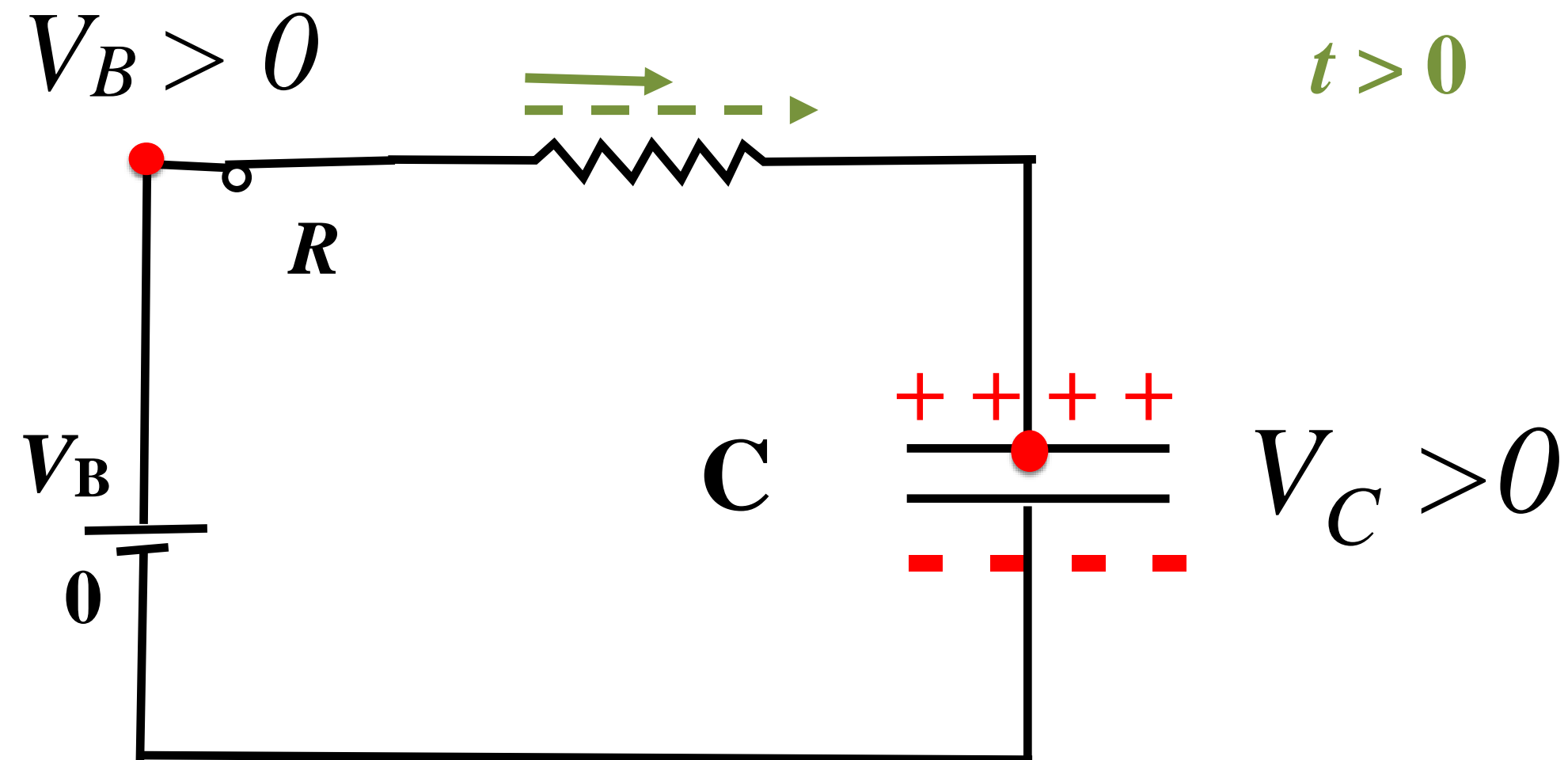

The current decreases from the beginning!

Charge a capacitor

voltage of battery
(constant)

voltage of capacitor
(a function of time)

$$I = \frac{V_B - V_C}{R} = \frac{\Delta Q}{\Delta t} \quad \leftarrow \text{increase of the charge on the capacitor}$$


$$V_C = \frac{Q}{C} \quad \leftarrow \text{a function of time}$$

$$\frac{\Delta Q}{\Delta t} = \frac{V_B - (Q/C)}{R} = \frac{-Q}{RC} + \frac{V_B}{R}$$

$$\tau = RC$$

Time constant of RC circuit
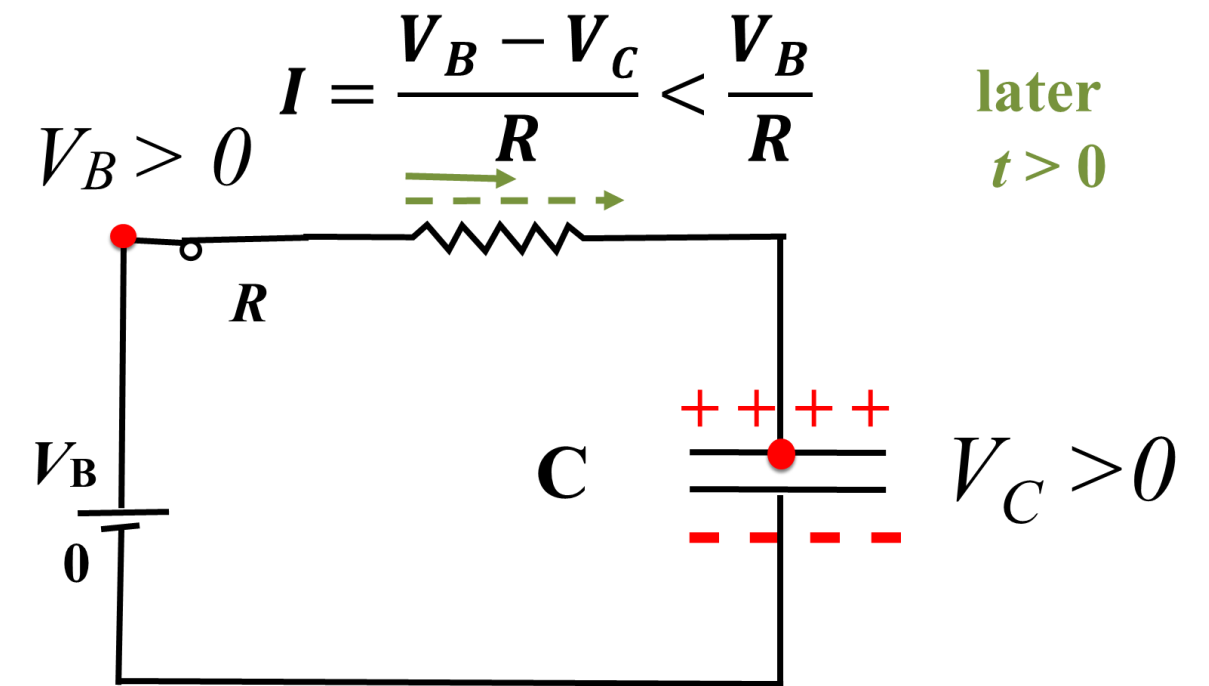
$$\Rightarrow \frac{dQ}{dt} = \frac{-Q}{\tau} + \frac{V_B}{R} \quad \text{differential equation!}$$



solution: $Q = \frac{\tau V_B}{R} - \frac{\tau V_B}{R} e^{-t/\tau}$

$$V_C = V_B (1 - e^{-t/RC})$$


Base for the natural logarithm

Charge a capacitor

$$V_C = V_B(1 - e^{-t/RC})$$

$$\tau = RC$$

*Time constant
of RC circuit*

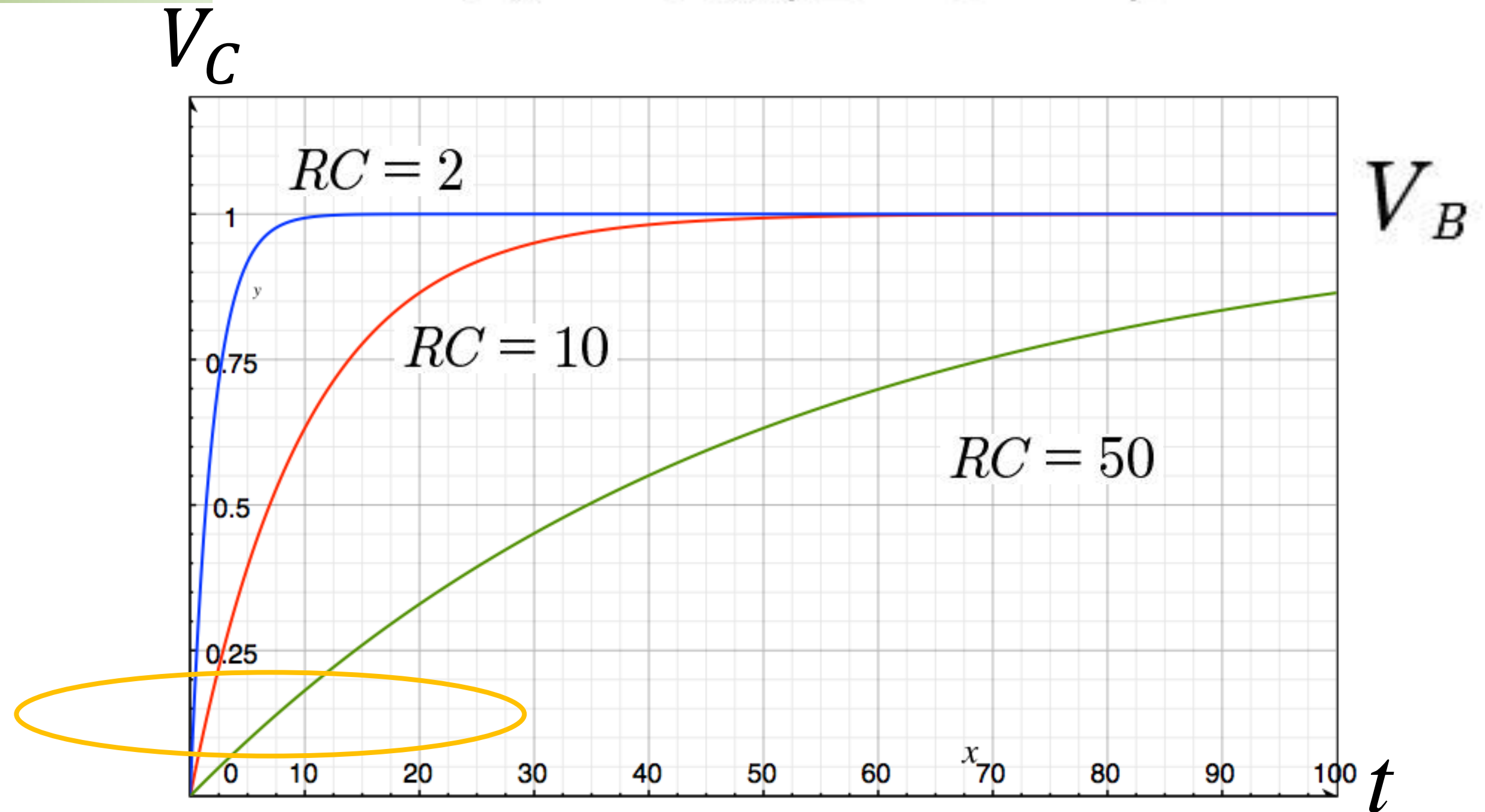

For small t :

$$e^{-t/RC} \approx 1 - (t/RC) \quad \Rightarrow \quad V_C \approx V_B \frac{t}{RC}$$


Current when charging

What is the current in R ?

$$I(t) = \frac{V_B - V_C(t)}{R}$$


$$V_C = V_B(1 - e^{-t/RC})$$

$$I(t) = \frac{V_B}{R} e^{-t/RC}$$

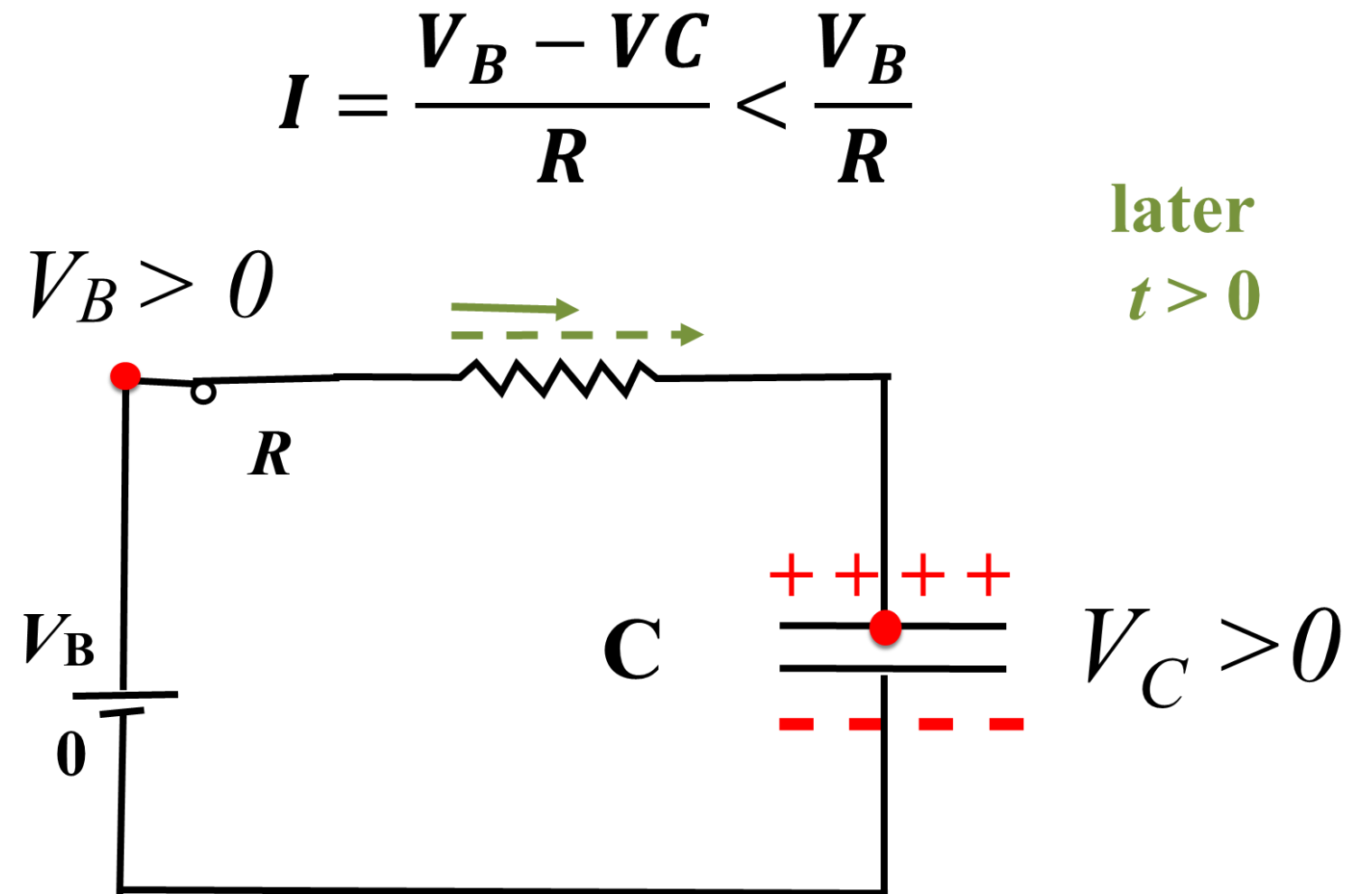

Current when charging

$I(t)$

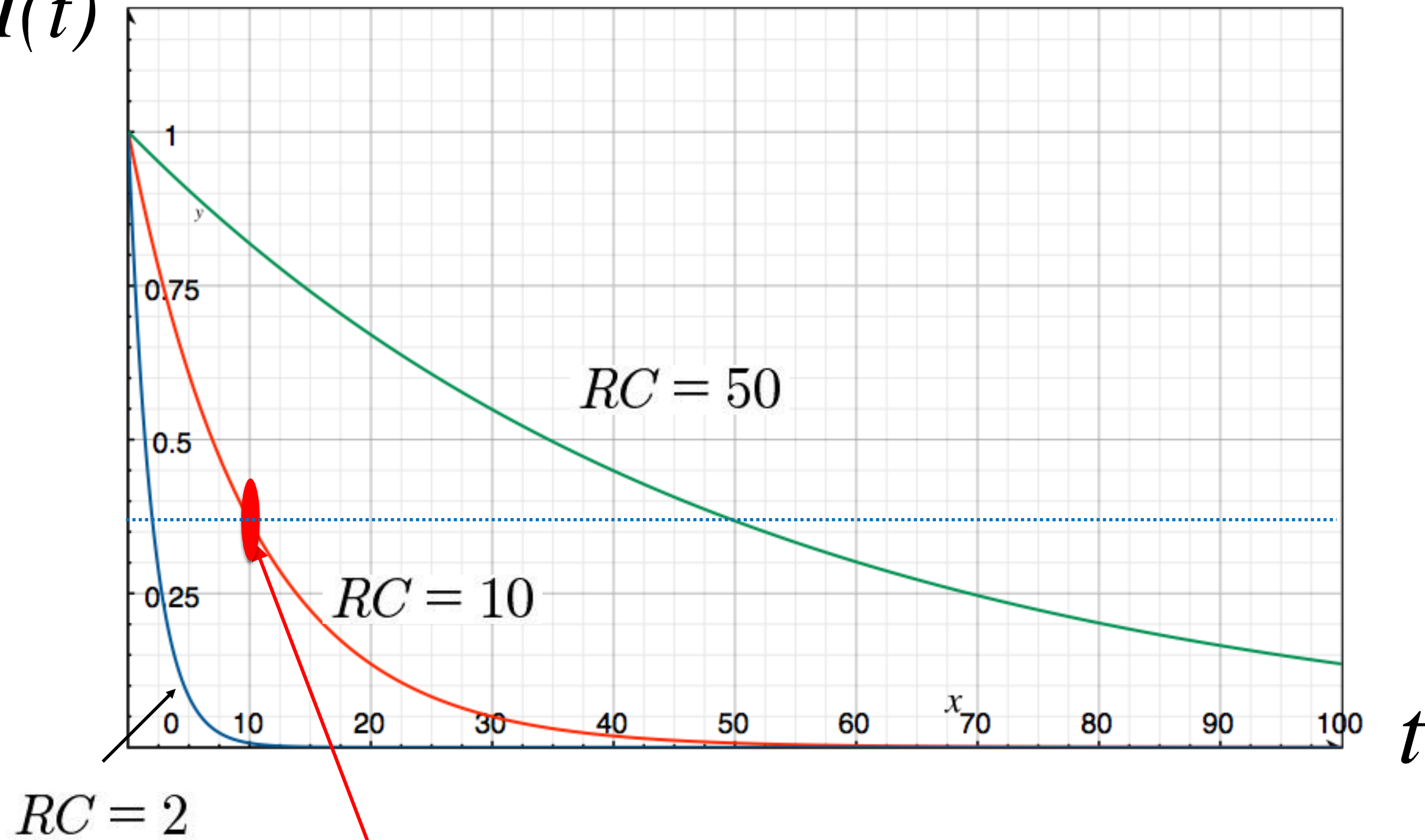

$$I(t) = \frac{V_B}{R} e^{-t/RC}$$

Exponential decay


At the $t = \text{time constant}$, the function decays to $1/e = 37\%$ of its original value

Discharging a capacitor

$$I = \frac{\Delta Q}{\Delta t} = \frac{-V_c}{R} = \frac{-Q}{RC}$$

negative sign because the current goes in the opposite direction (removing charges on the capacitor)
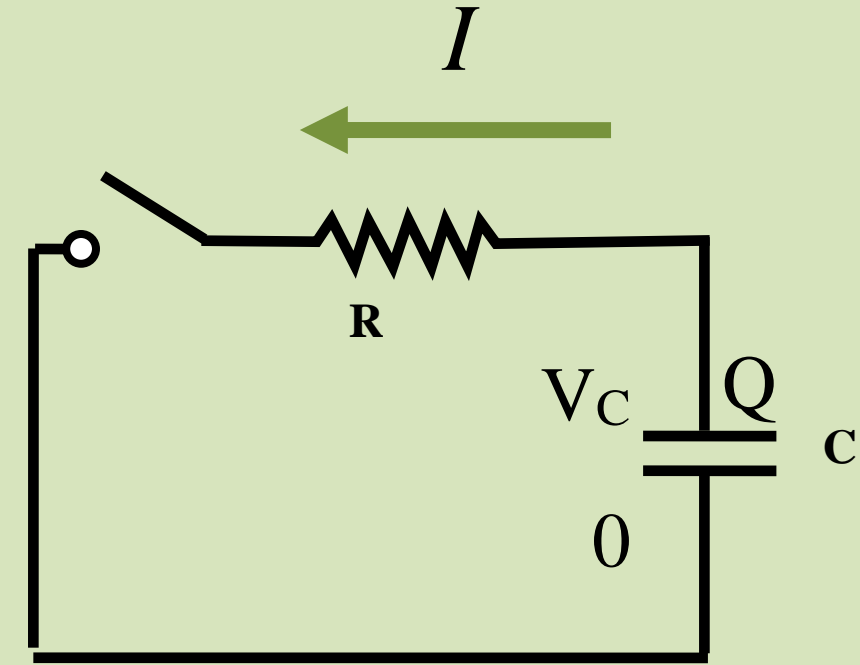
$$\Rightarrow \frac{dQ}{dt} = \frac{-Q}{\tau}$$




solution: $Q(t) = Q_0 e^{-t/RC}$

$$Q_0 = Q(0) = C V_c$$

$$V(t) = \frac{Q(t)}{C} = V_c e^{-t/RC}$$


Discharging a capacitor

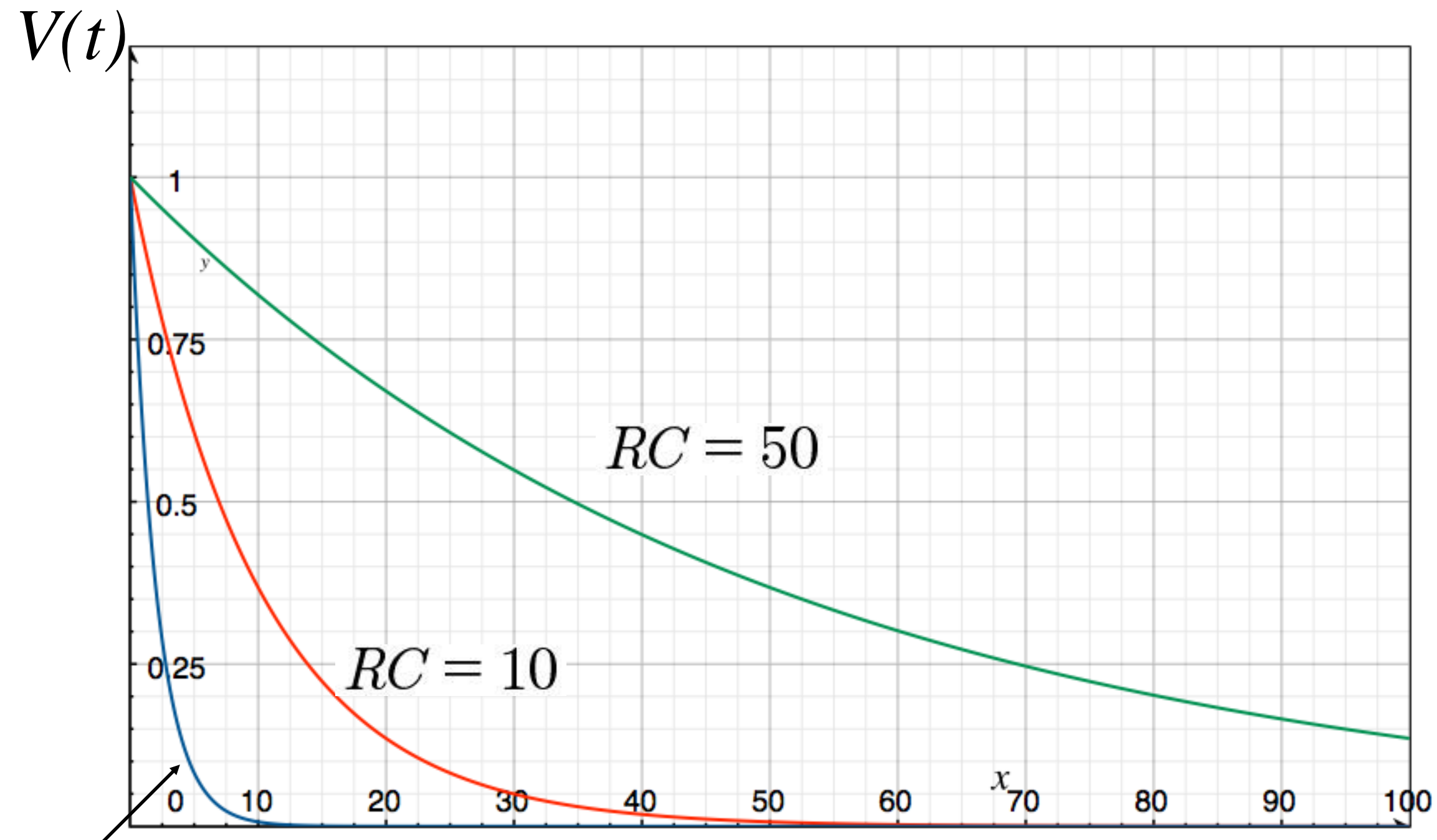

$RC = 2$

Exponential decay

Discharging a capacitor

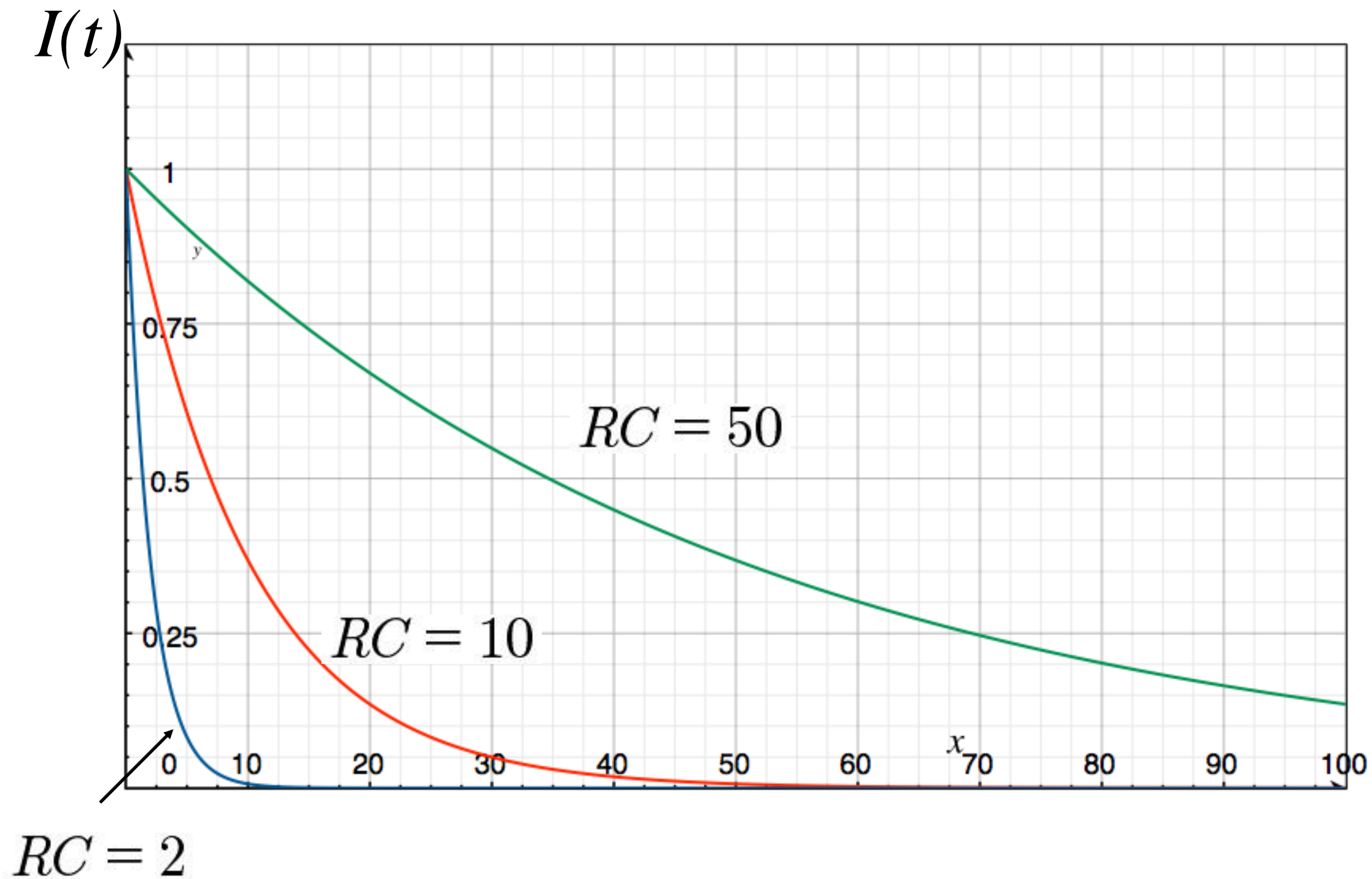

Exponential decay

Capacitors' application

