
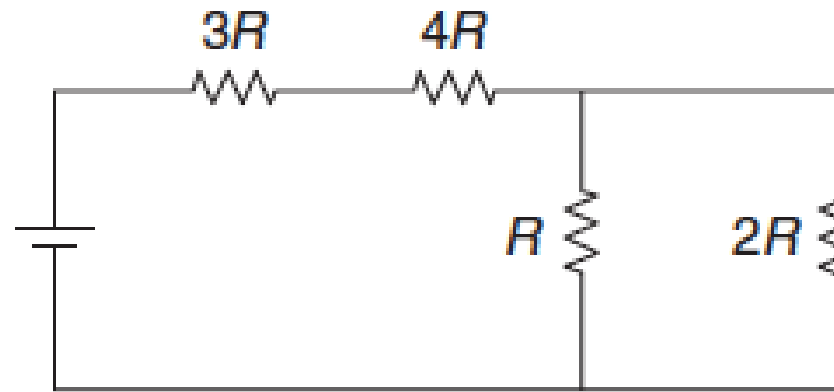


Exercise 3

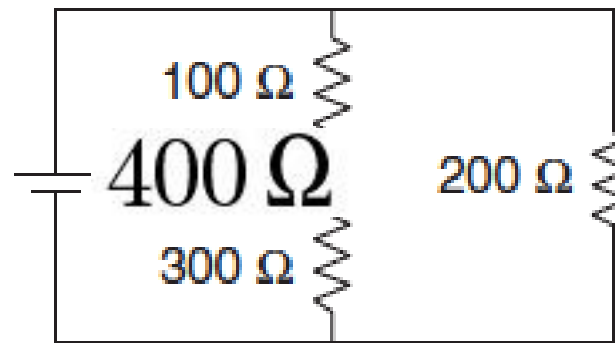

1. The figure above shows four resistors connected in a circuit with a battery. Which of the following correctly ranks the potential difference, ΔV , across the four resistors?
- (A) $\Delta V_{4R} > \Delta V_{3R} > \Delta V_{2R} > \Delta V_R$
- (B) $\Delta V_{4R} > \Delta V_{3R} > \Delta V_{2R} = \Delta V_R$ ✓ ■ B
- (C) $\Delta V_{4R} = \Delta V_{3R} > \Delta V_R > \Delta V_{2R}$
- (D) $\Delta V_{2R} = \Delta V_R > \Delta V_{3R} > \Delta V_{4R}$



2. The figure above shows three resistors connected in a circuit with a battery. Which of the following correctly ranks the energy E dissipated in the three resistors during a given time interval?

(A) $E_{300\Omega} > E_{200\Omega} > E_{100\Omega}$

(B) $E_{300\Omega} > E_{100\Omega} > E_{200\Omega}$

(C) $E_{200\Omega} > E_{300\Omega} > E_{100\Omega}$ ✓ ■

(D) $E_{200\Omega} > E_{100\Omega} > E_{300\Omega}$

$$P = \frac{V^2}{R_{eq}}$$

$$P_{100+300} < P_{200}$$

$$P = RI^2$$

$$\Rightarrow P_{100} < P_{300}$$

$$\Rightarrow P_{200} > P_{300} > P_{100} \quad \text{(C)}$$

If two household lightbulbs rated 60W and 100W are connected in series to household power, which will be brighter?

$$P = \frac{V^2}{R}$$

$$\frac{V_{plug}^2}{R_{100W}} = 100 \text{ W} \implies R_{100W} = \frac{V_{plug}^2}{100}$$

$$R_{60W} = \frac{V_{plug}^2}{60}$$

$$\frac{R_{100W}}{R_{60W}} = \frac{60}{100} = 0.6$$

The 100 W bulb has a lower resistance

Connected in series: the current is the same

$$P = RI^2 \quad \text{current is the same} \implies P_{100W} < P_{60W}$$


What is the difference between resistance and resistivity?

- (a) Resistance is a property of the material, while resistivity depends on the amount, size, and shape of the material.
- ✓ (b) Resistivity is a property of the material, while resistance depends on the amount, size, and shape of the material.
- (c) Resistance is a property of ohmic devices, while resistivity is a property of non-ohmic devices.
- (d) Resistivity is a property of ohmic devices, while resistance is a property of non-ohmic devices.

A set of resistors is placed in series with a source of constant potential difference. Which of the following must be the same for each resistor?


- ✓ (a) Potential difference across it
- (b) Current through it
- (c) Power dissipated in it
- (d) Resistance of it

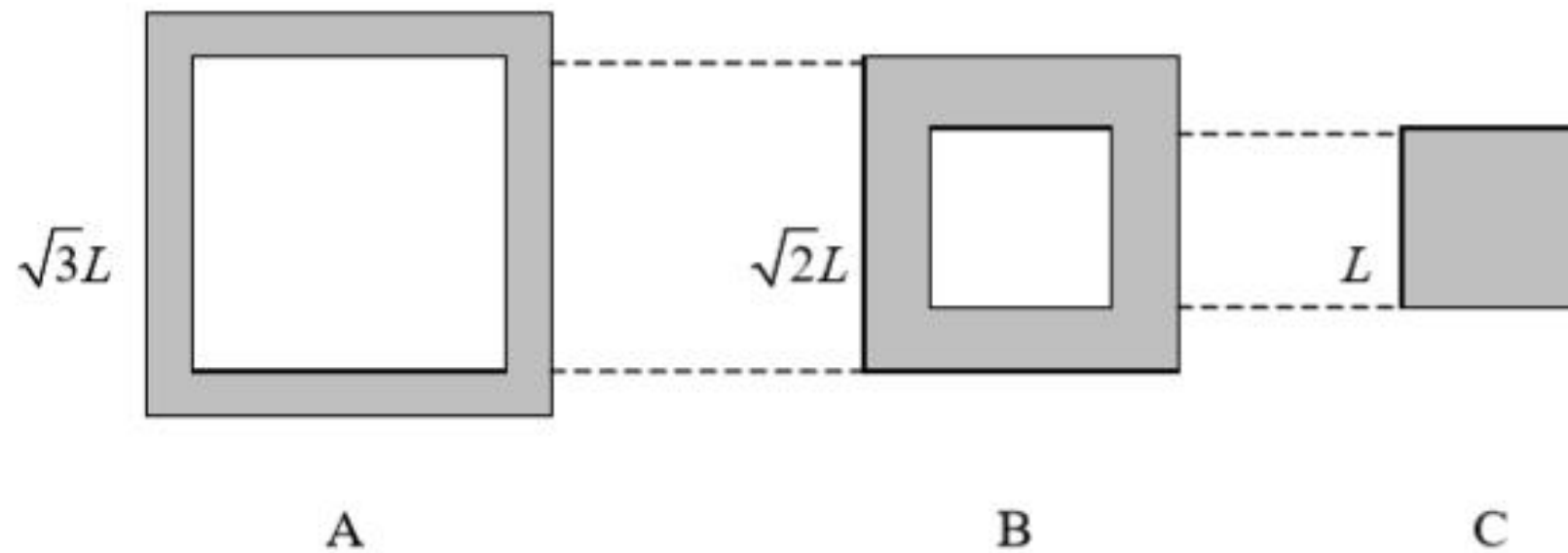The figure below shows cross sections through three long conductors of the same length and material, with square cross-sections of edge as shown. Conductor B will fit snugly within conductor A, and conductor C will fit snugly within conductor B. Rank the three conductors according to their end-to-end resistance, greatest first.



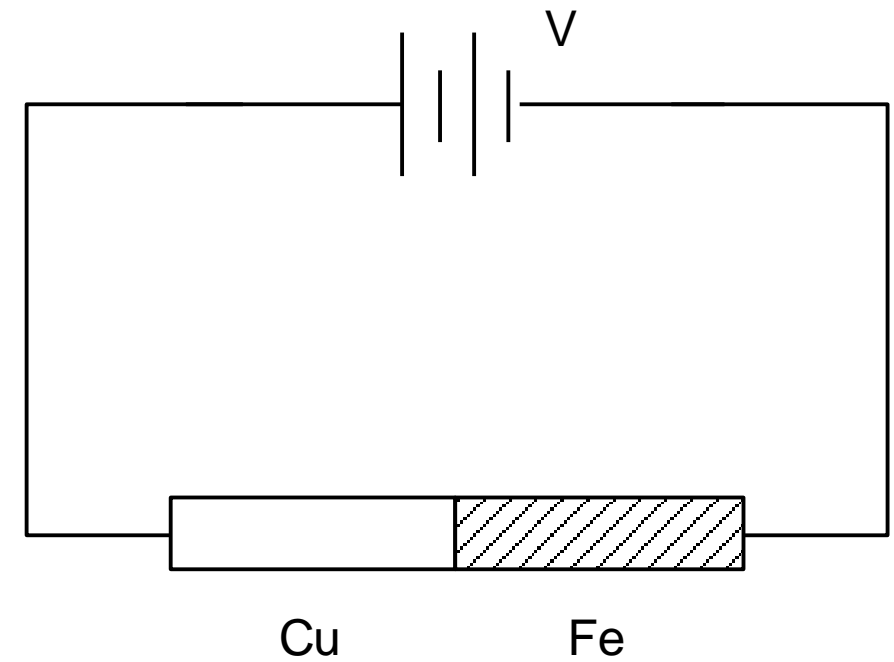- (A) A - B - C (Conductor A has the greatest resistance, and conductor C has the least resistance.)
- (B) A - C - B
- (C) B - A - C
- (D) B - C - A
- (E) C - A - B
- (F) C - B - A
- (G) All three have the same resistance. ✓

A copper rod and an iron rod are joined end-to-end and connected to a voltage source, as shown in the graph. Both rods have a cross-sectional area of 0.01 cm^2 . Each is 1 meter long. Which of the following statements are correct?



- (1) The copper rod dissipates more electric power than the iron rod
- (2) The iron rod has a greater potential drop than the copper rod has
- (3) Free electrons move from iron to copper

<2 3>

The current in the 6-ohm resistor in the circuit is 0.5 ampere. The voltage V applied to the circuit is


(A) 6 V

(B) 10 V

(C) 18 V ✓

(D) 24 V


(E) 27 V

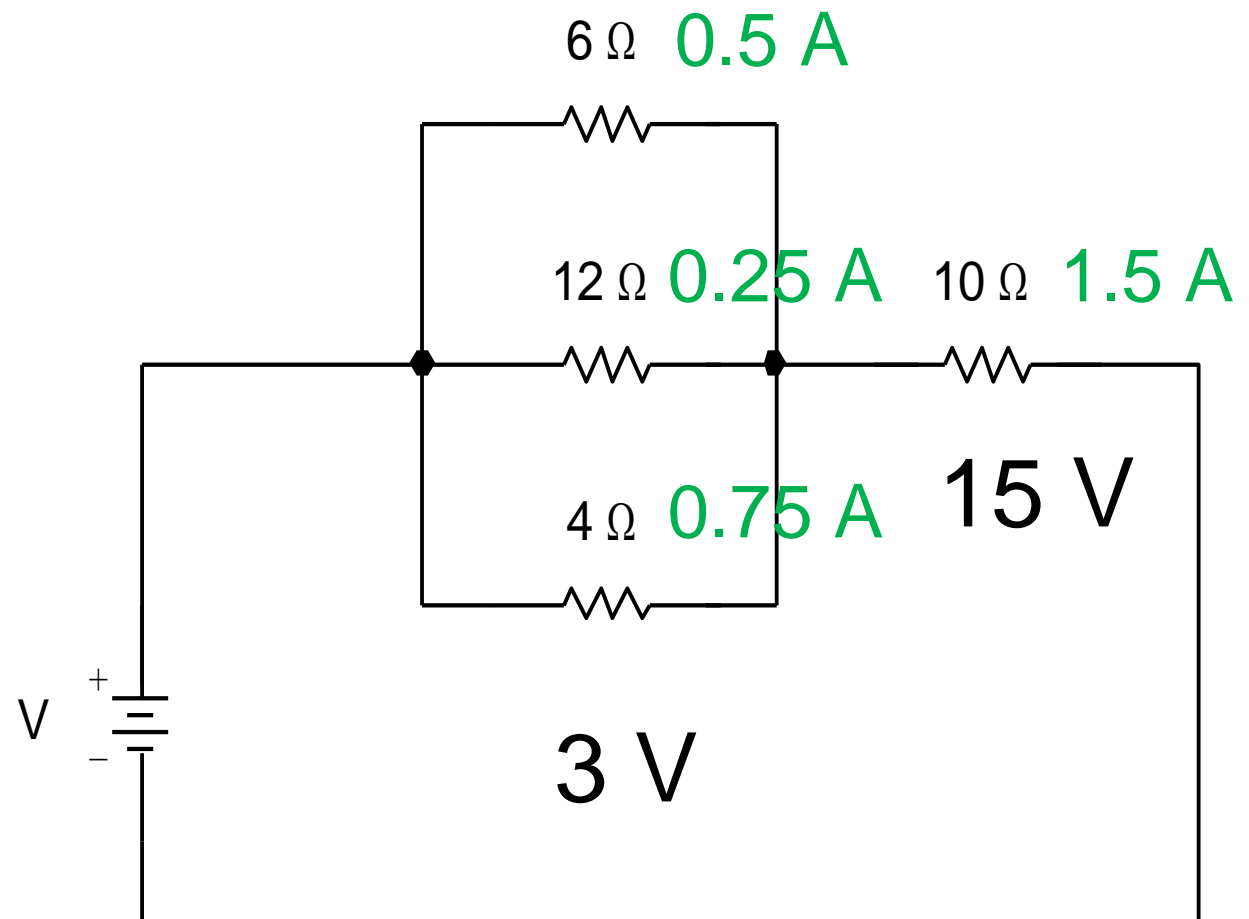

(C)

Which of the following equations is a valid Kirchhoff current equation for the circuit?

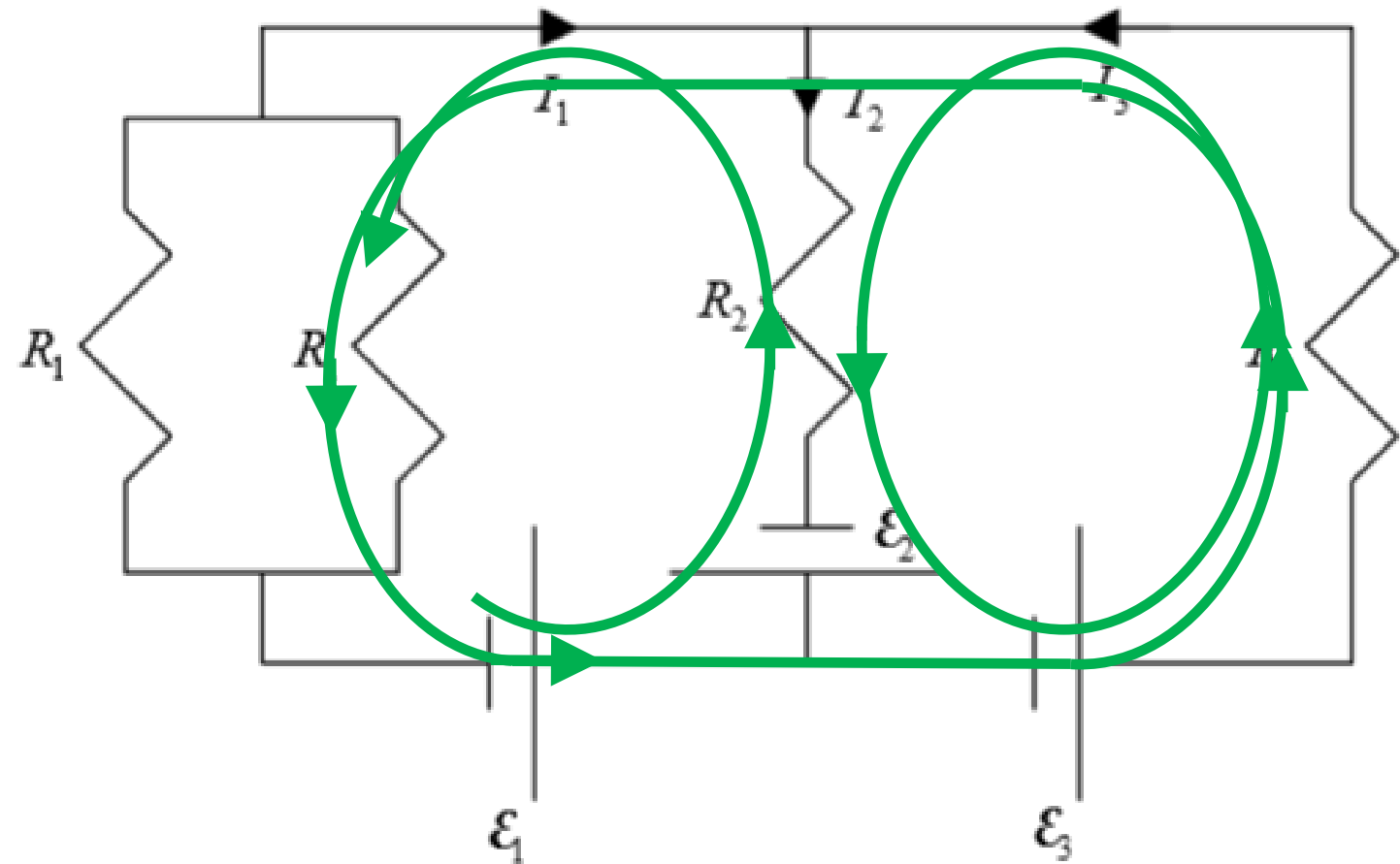
- (A) $I_1 + I_2 + I_3 = 0$
- (B) $I_1 + I_2 = I_3$
- ✓ (C) $I_1 + I_3 = I_2$
- (D) $I_2 + I_3 = I_1$
- (E) none of the above



Which of the following equations is **not** a valid Kirchhoff voltage equation for the circuit?

- ✓ (A) $+\mathcal{E}_1 - \mathcal{E}_2 + I_2 R_2 + I_1 R_1 = 0$
- (B) $+\mathcal{E}_1 + \mathcal{E}_3 - I_3 R_3 + \frac{1}{2} I_1 R_1 = 0$
- (C) $+\mathcal{E}_2 + \mathcal{E}_3 - I_3 R_3 - I_2 R_2 = 0$

Find the currents flowing in the circuit

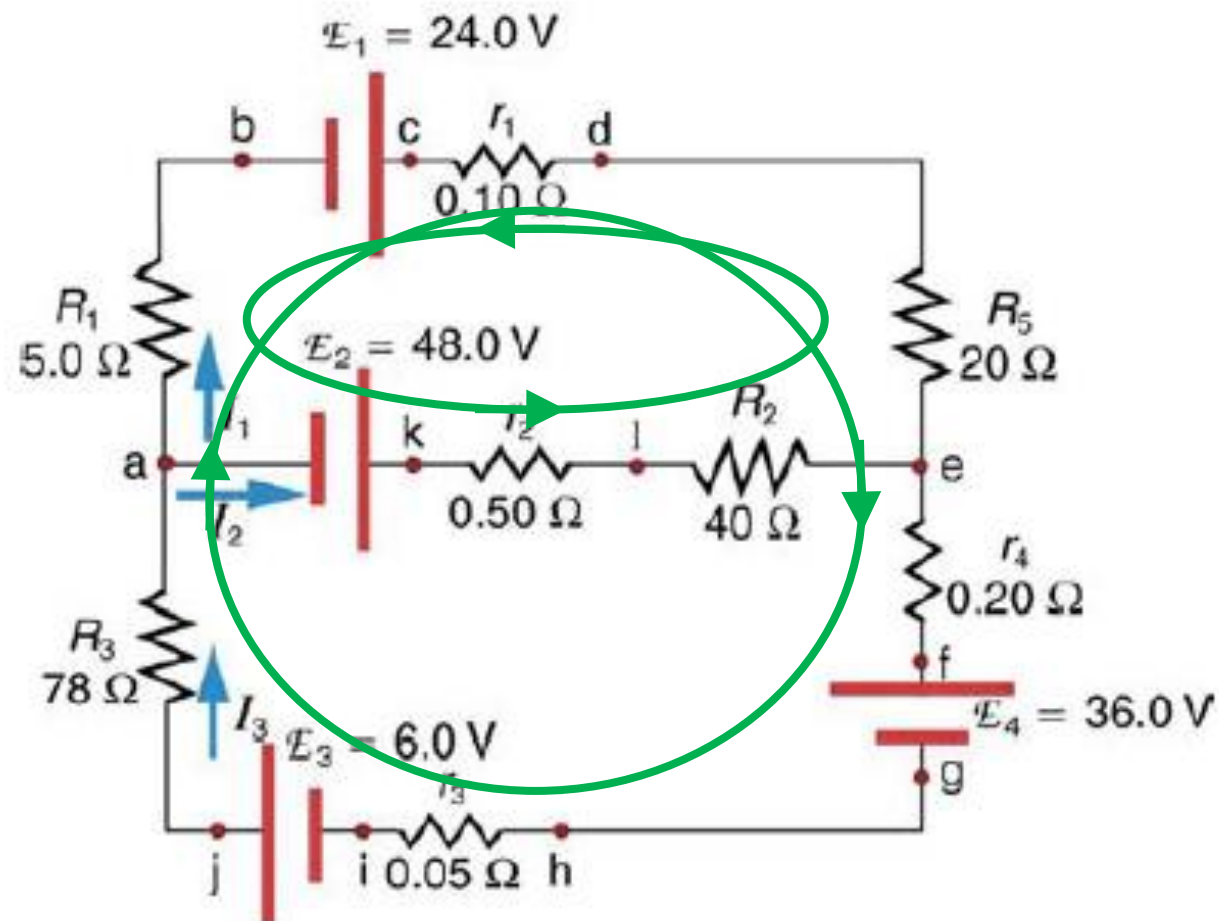


$$\begin{cases} I_1 = -0.345 \text{ A} \\ I_2 = 0.379 \text{ A} \\ I_3 = 0.036 \text{ A} \end{cases}$$


$$I_3 = I_1 + I_2$$

$$\mathcal{E}_2 - r_2 I_2 - R_2 I_2 + R_5 I_1 + r_1 I_1 - \mathcal{E}_1 + R_1 I_1 = 0$$

$$-R_1 I_1 + \mathcal{E}_1 - r_1 I_1 - R_5 I_1 - R_4 I_3 - \mathcal{E}_4 - r_3 I_3 + \mathcal{E}_3 - R_3 I_3 = 0$$

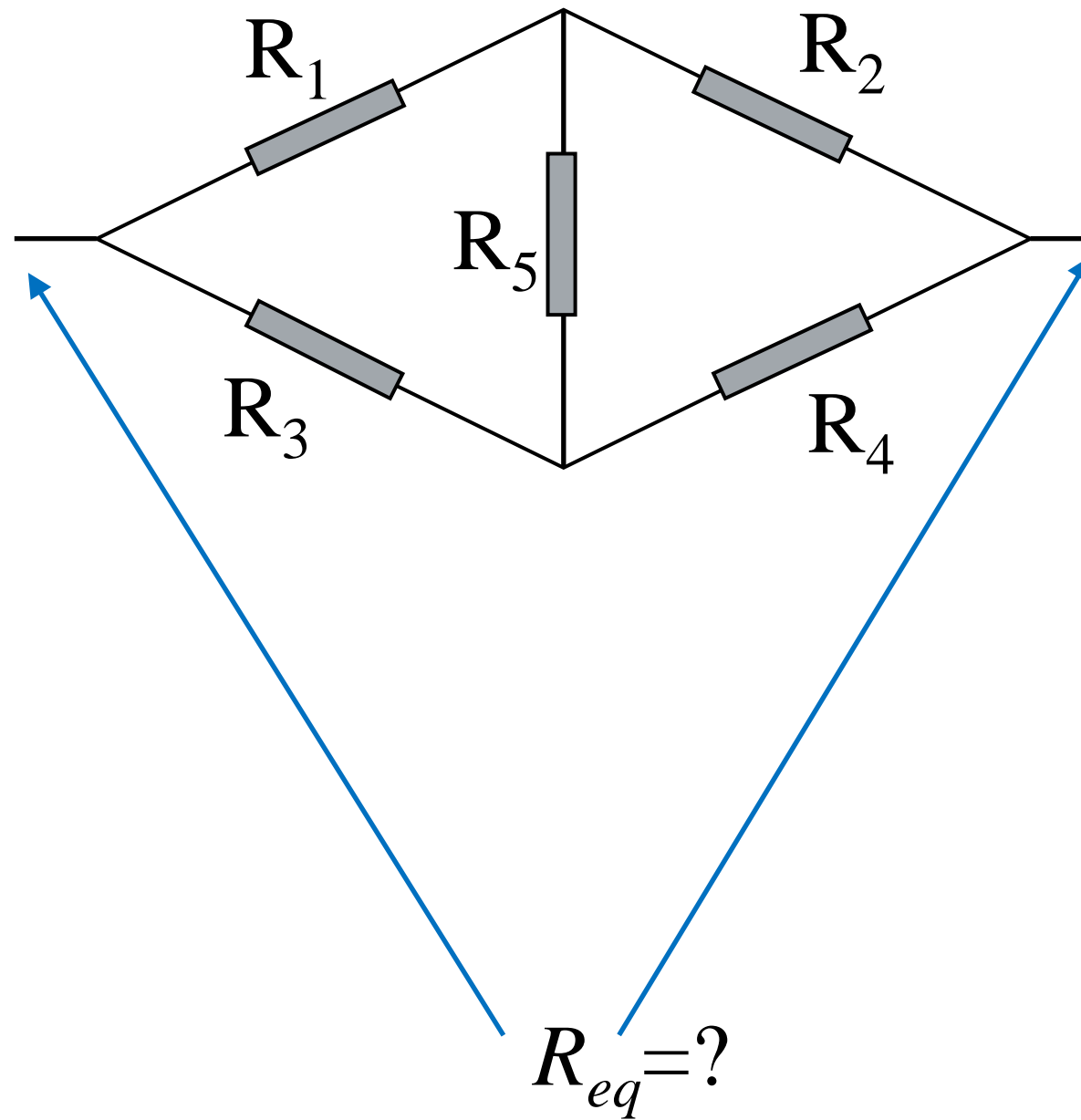A (resistance) bridge circuit – what is the equivalent resistance?



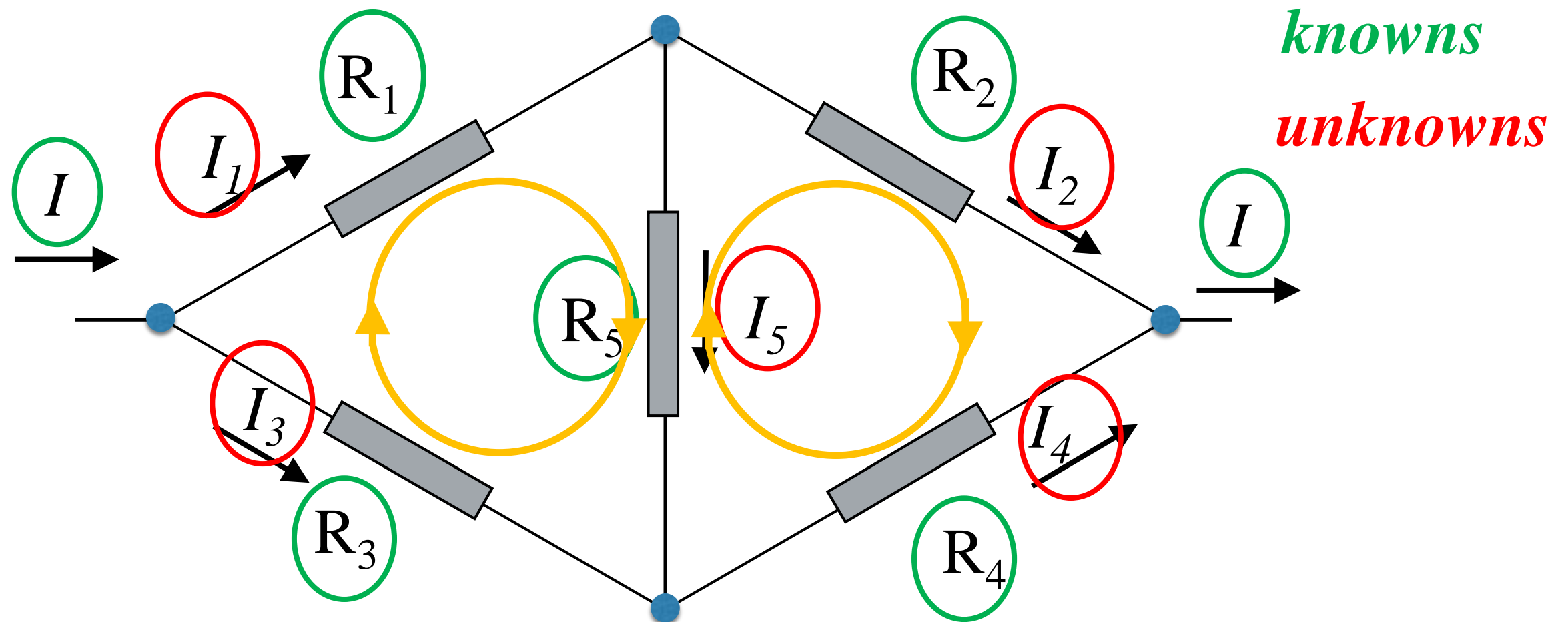

Junctions:

$$I = I_1 + I_3$$

$$I = I_2 + I_4$$

$$I_5 = I_1 - I_2$$

$$I_5 = I_4 - I_3 \quad \text{---} \textit{dependent}$$

loops:

$$-R_1 I_1 - R_5 I_5 + R_3 I_3 = 0$$


$$-R_2 I_2 + R_4 I_4 + R_5 I_5 = 0$$

$$R_{eq} = \frac{I_1 R_1 + I_2 R_2}{I}$$

$$R_{eq} = \frac{R_1 R_2 R_3 + R_1 R_3 R_4 + R_1 R_3 R_5 + R_1 R_4 R_5 + R_1 R_2 R_4 + R_2 R_3 R_5 + R_2 R_4 R_5 + R_2 R_3 R_4}{R_1 R_2 + R_1 R_4 + R_1 R_5 + R_2 R_5 + R_5 R_4 + R_2 R_3 + R_3 R_4 + R_3 R_5}$$

20. A car battery with a 12-V emf and an internal resistance of $0.050\ \Omega$ is being charged with a current of 60 A. Note that in this process the battery is being charged.

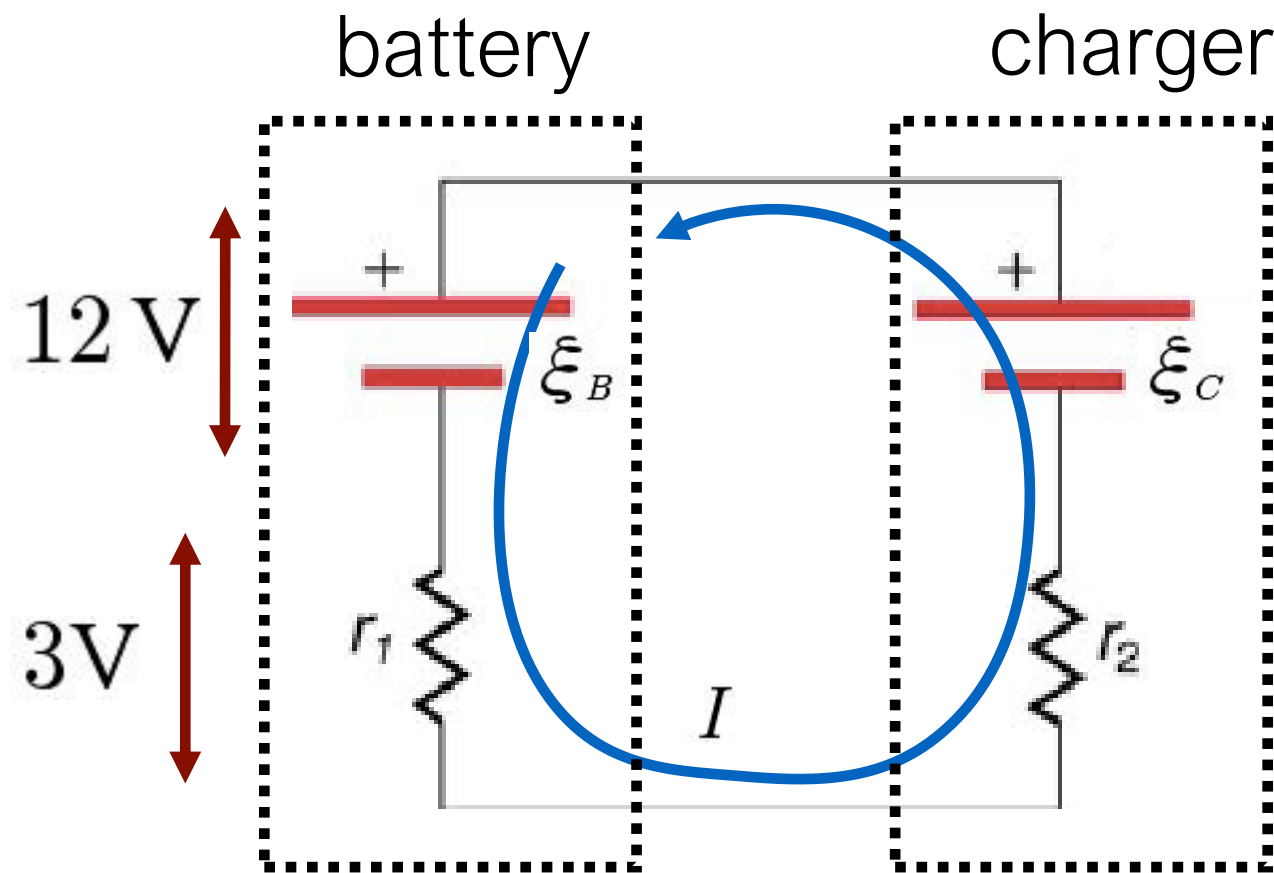(a) What is the potential difference across its terminals?



$$\xi = 12\text{ V}$$

$$r_1 = 0.05\ \Omega$$


$$I = 60\text{ A}$$

$$r_1 I = 0.05\ \Omega \times 60\text{ A} = 3\text{ V}$$

$$V = 12\text{ V} + 3\text{ V} = 15\text{ V}$$

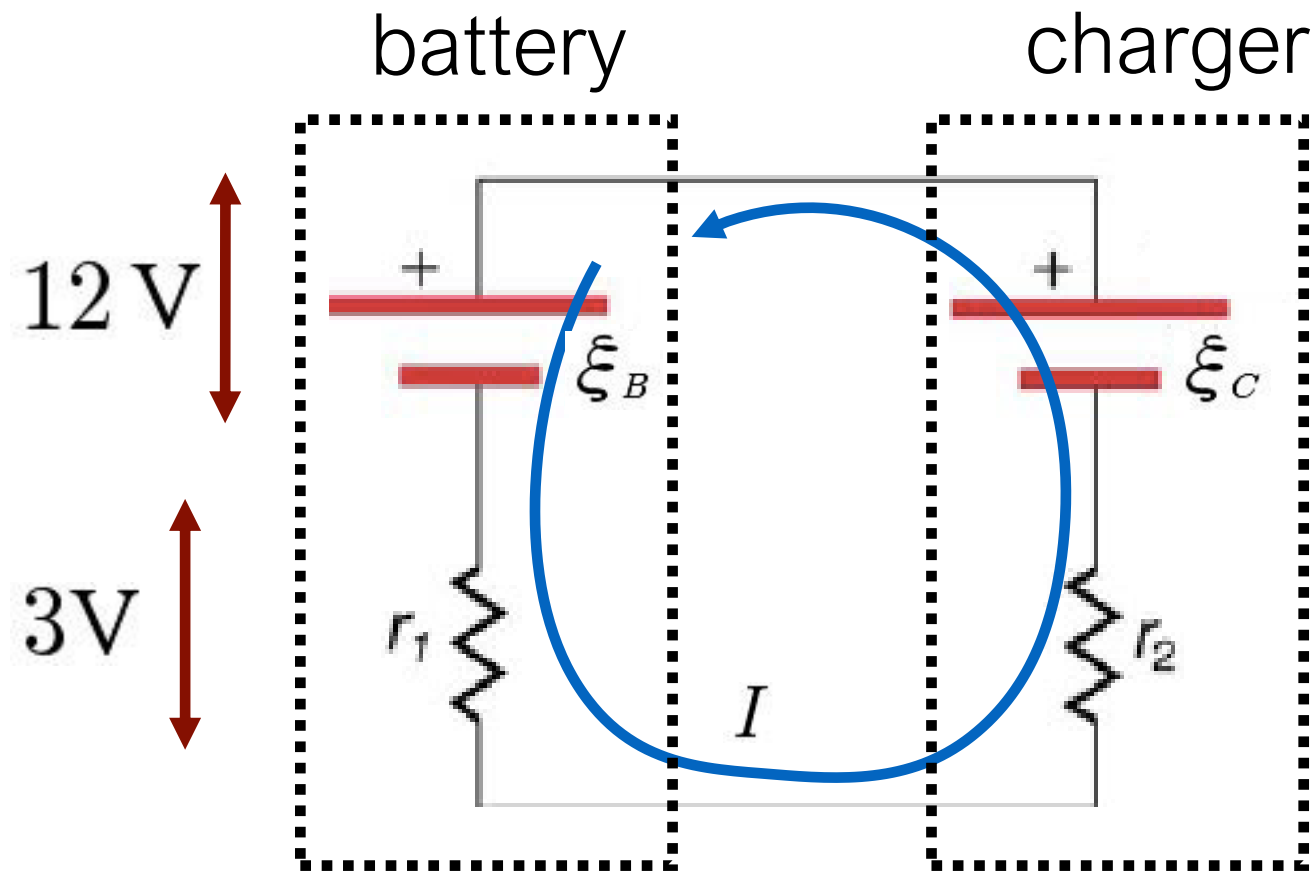(b) At what rate is thermal energy being dissipated in the battery?

$$P_{r_1} = (r_1 I) I = 0.05\ \Omega \times (60\text{ A})^2 = 180\text{ W}$$




(c) At what rate is electric energy being converted to chemical energy?

current inside the battery: $I = 60\text{ A}$

potential difference inside the battery: $V = 12\text{ V}$

$$P_{\text{batt}} = 12\text{ V} \times 60\text{ A} = 720\text{ W}$$

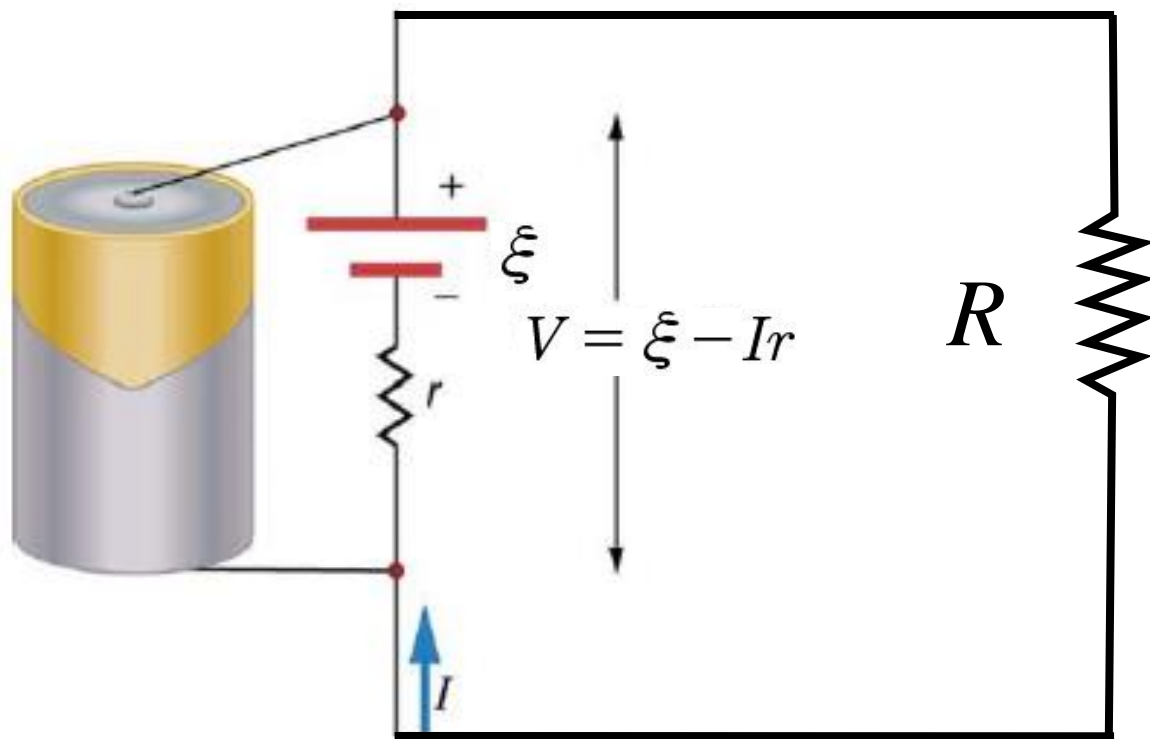(d) What are the answers to (a) and (b) when the battery is used to supply 60 A to the starter motor?



$$I = 60 \text{ A}$$

$$\xi = 12 \text{ V}$$

$$r_1 = 0.05 \Omega$$

potential difference across the terminals:


$$V = \xi - Ir_1 = 12 \text{ V} - (60 \text{ A}) 0.05 \Omega = 9 \text{ V}$$

thermal energy dissipated in the battery:


$$P = r_1 I^2 = 0.05 \Omega \times (60 \text{ A})^2 = 180 \text{ W}$$

24. A child's electronic toy is supplied by three 1.58-V alkaline cells having internal resistances of $0.0200\ \Omega$ in series with a 1.53-V carbon-zinc dry cell having a $0.100\text{-}\Omega$ internal resistance. The load resistance is $10.0\ \Omega$.

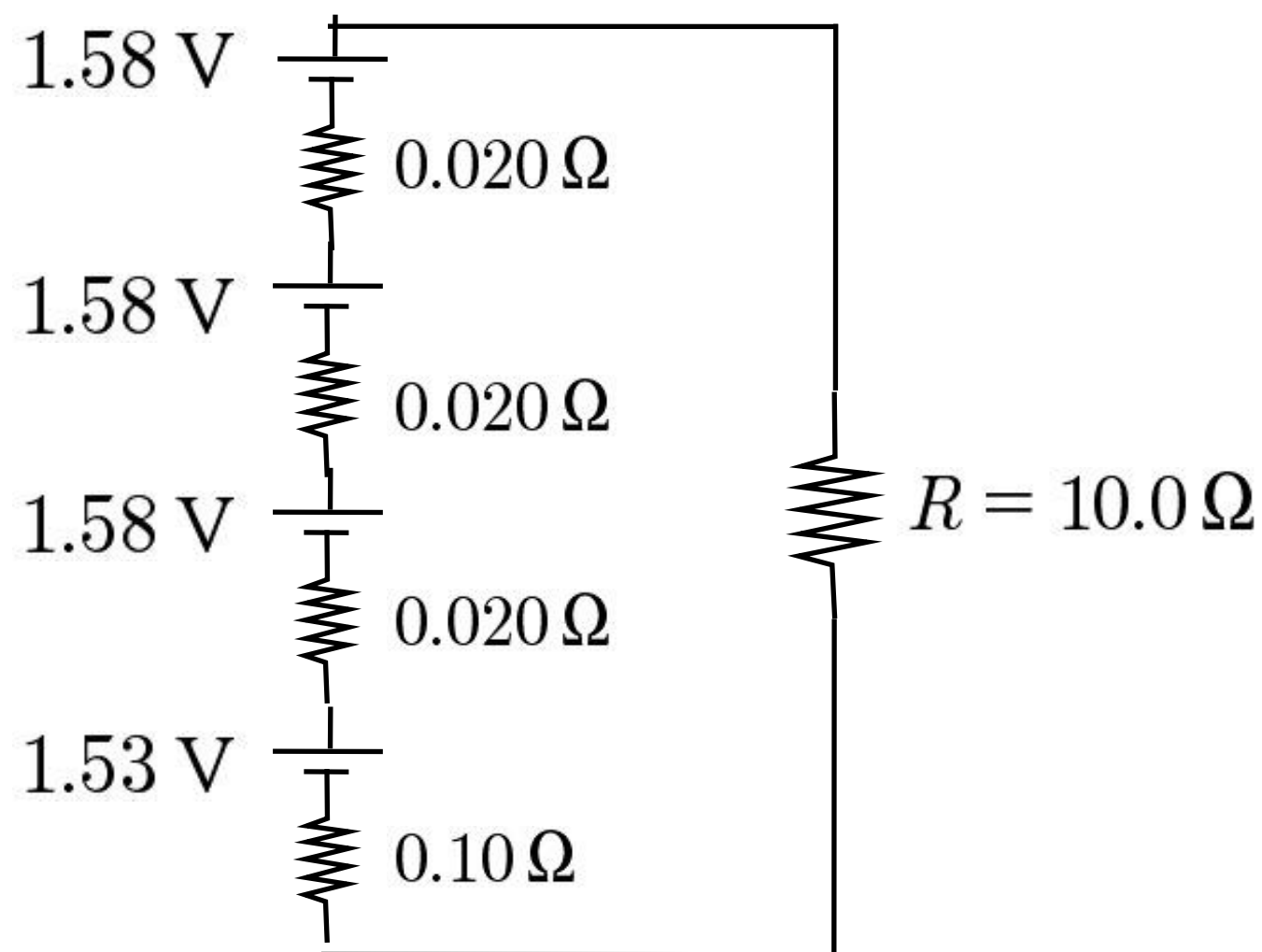(a) Draw a circuit diagram of the toy and its batteries



(b) What current flows?

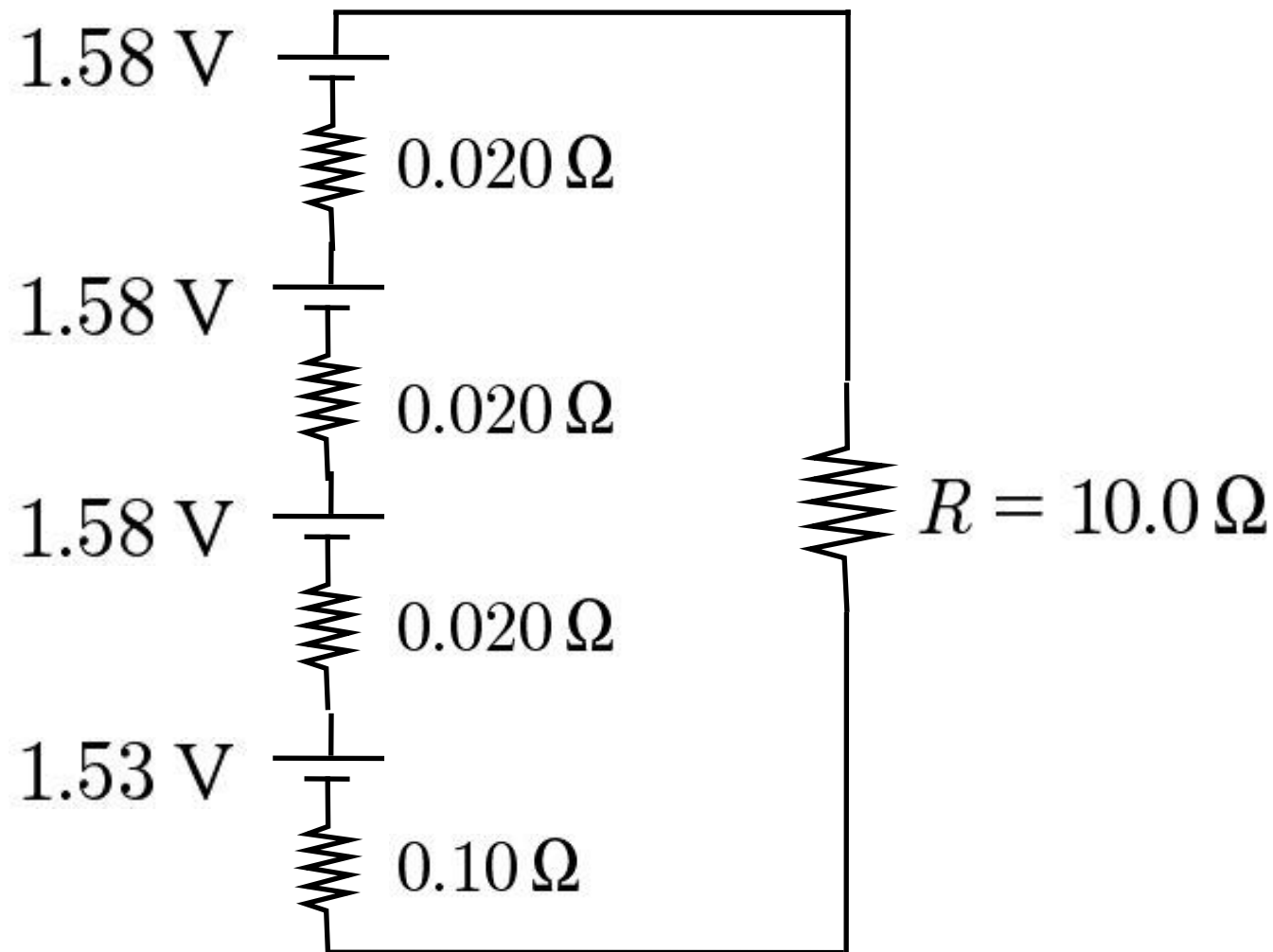


$$\xi_{tot} = (3 \times 1.58 \text{ V}) + 1.53 \text{ V} = 6.27 \text{ V}$$

$$R_{tot} = (3 \times 0.02 \Omega) + 0.1 \Omega + 10 \Omega = 10.16 \Omega$$

$$I = \frac{6.27 \text{ V}}{10.16 \Omega} = 0.62 \text{ A}$$

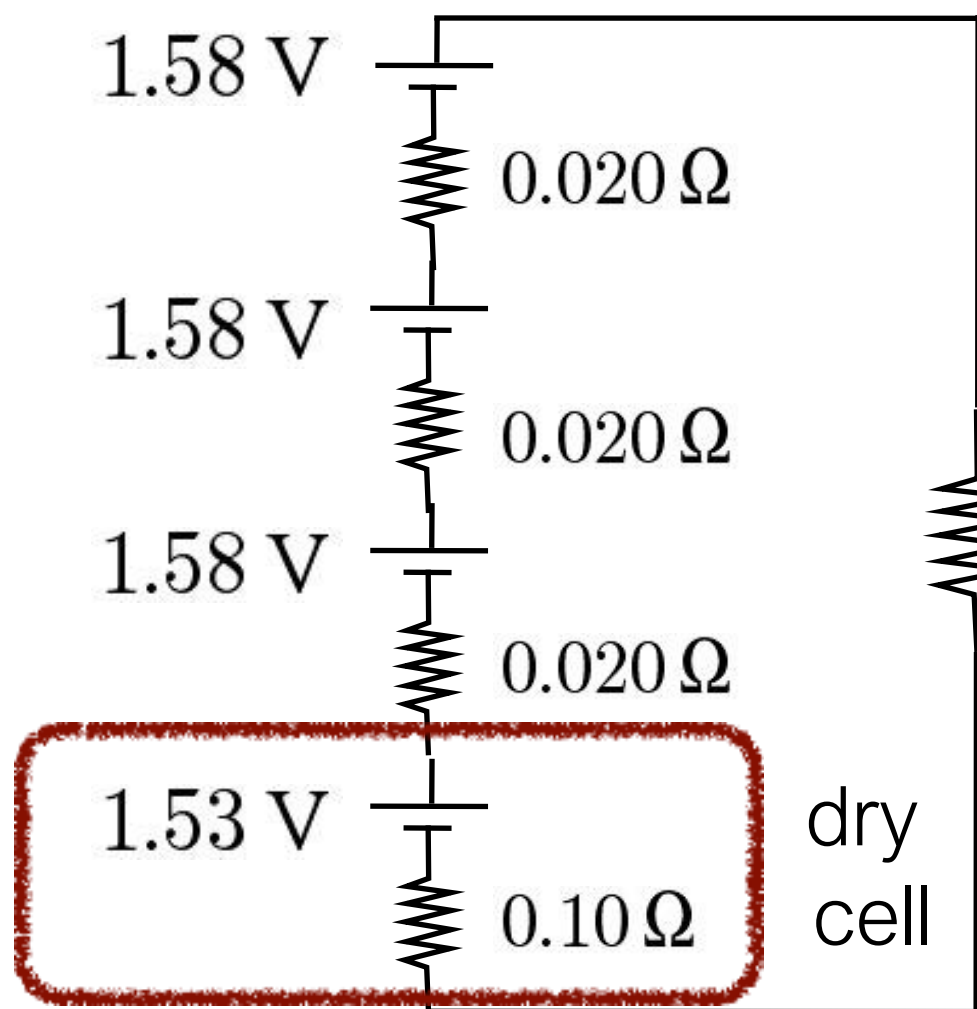(c) How much power is supplied to the load?



$$I = 0.62 \text{ A}$$

$$P_{load} = RI^2 = 10.0 \Omega (0.62 \text{ A})^2 = 3.8 \text{ W}$$

(d) What is the internal resistance of the dry cell if it goes bad, resulting in only 0.500 W supplied to the load?

$$P = RI^2 = 0.5 \text{ W}$$

$$I = 0.22 \text{ A}$$

$$R_{tot} = (10.06 \Omega + r) = \frac{\mathcal{E}}{I} = 28.12 \Omega$$

$$r = 18.06 \Omega$$

A battery having an EMF of 3.0 V and an internal resistance of $0.1\ \Omega$ is used to power a light bulb, which consumes an electric power of 5.6 W . Now another identical light bulb is connected to the battery, in parallel with the first light bulb. What is the total power consumed by the two light bulbs?

(A) 13.5 W

(B) 11.2 W

(C) 9.8 W

(D) 5.4 W

$$P_1 = \frac{\mathcal{E}^2}{R} \left(\frac{R}{r + R} \right)^2$$

$$5.6 = \frac{3^2}{R} \left(\frac{R}{0.1 + R} \right)^2 \quad R = 1.4\ \Omega$$

$$P_2 = \frac{2\mathcal{E}^2}{R} \left(\frac{R}{2r + R} \right)^2 \approx 9.8\text{ W}$$

(C)